

Chapter # 1: Introduction

Contemporary Logic Design

Randy H. Katz
University of California, Berkeley

May 1993


Motivation

Dramatic Change in the Way Industry Does Hardware Design

- *Pervasive use of Computer-Aided Design Tools*
 - Deemphasis on hand design methods
 - Emphasis on abstract design representations
 - Hardware design begins to look like software design
- *Emergence of Rapid Implementation Circuit Technology*
 - Programmable rather than discrete logic
- *Importance of Sound Design Methodologies*
 - Synchronous Designs
 - Rules of Composition

The Elements of Modern Design

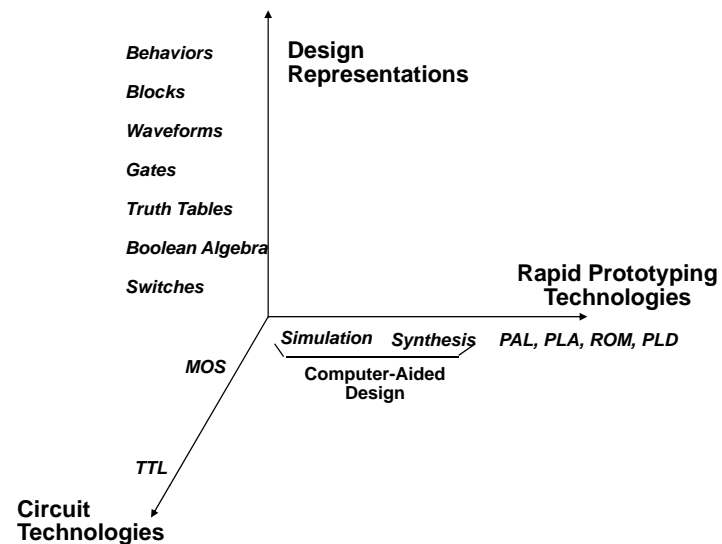Representations, Circuit Technologies, Rapid Prototyping




Chapter Overview

- Process of Design
- Digital Systems
- Design Representations
- Rapid Prototyping

The Process Of Design

Contemporary Logic Design
Introduction

 

Design

Initial concept: what is the function performed by the object?
Constraints: How fast? How much area? How much cost?
Refine abstract functional blocks into more concrete realizations

Implementation

Assemble primitives into more complex building blocks
Composition via wiring
Choose among alternatives to improve the design

Debug

Faulty systems: design flaws, composition flaws, component flaws
Design to make debugging easier
Hypothesis formation and troubleshooting skills

© R.H. Katz Transparency No. 1-5

The Art Of Design: Refinement of Representations

Contemporary Logic Design
Introduction

1. Functional Specification/What the System Does

Ex: Traffic Light Controller


Lights point in the directions N, S, E, W

Illuminates the same lights N as S and E as W

Cycles thru the sequence GREEN-YELLOW-RED

N-S and E-W never GREEN or YELLOW at the same time

 Stay GREEN for 45 seconds, yellow for 15, red for 60



2. Performance Constraints/Requirements to be Met

speed: compute changes in under 100 ms

power: consume less than 20 watts

area: implementation in less than 20 square cm

cost: less than \$20 in manufacturing costs

© R.H. Katz Transparency No. 1-6

The Art of Design: "To Design Is To Represent"

Contemporary Logic Design
Introduction

1. English language specification

easy to write, but not precise and subject to ambiguity

2. Functional description

more precise specification


flow charts, program fragments

3. Structural description

complex components decomposed into
compositions of less complex components

 4. Physical description

the design in terms of most primitive
building blocks, e. g., logic gates or
transistors



© R.H. Katz Transparency No. 1-7

The Process of Design

Contemporary Logic Design
Introduction

Implementation as Assembly

Top Down Design:

Complex functions replaced by more primitive functions

Bottom Up Design:

Primitives composed to build more and more complex assemblies

Rules of Composition and Correctness by Construction:

Electrical Rules: how many components can be cascaded?

Timing Rules: how does the system change in conjunction with
periodic triggering events?


© R.H. Katz Transparency No. 1-8

The Process of Design

Top Down Decomposition

Contemporary Logic Design
Introduction

Structural Representation

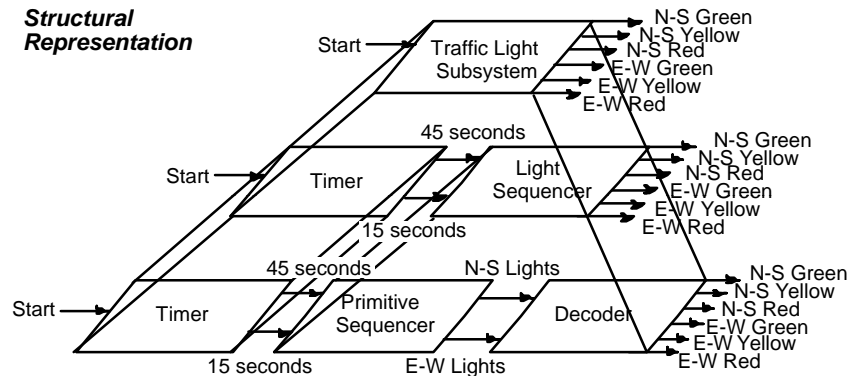

To decomposition of high level functions into more primitive functions

© R.H. Katz Transparency No. 1-9

The Process of Design

Bottom Up Assembly

Contemporary Logic Design
Introduction

Primitives composed to build
more and more complex assemblies

e.g., a group of rooms form a floor

e.g., a group of floors form a bldg.

a group of transistors form a gate

a group of gates form an addition circuit

addition circuits plus storage circuits
form a processor datapath

Building

Floor

Rooms

© R.H. Katz Transparency No. 1-10

The Process of Design: Debugging the System

What Can Go Wrong

Contemporary Logic Design
Introduction

• **Design Flaws**

Implementation does not meet functional specification

Logic design is incorrect (wrong function implemented)

Misinterpretation or corner cases ignored

• **Implementation Flaws**

Individual modules function correctly but their compositions do not

Misunderstanding of interface and timing behavior

Wiring mistakes, Electrical mistakes

• **Component Flaws**

Logically correct and correctly wired

Not all hardware components are guaranteed to work!

E.g., burnt out component

© R.H. Katz Transparency No. 1-11

The Process of Design

Debugging via Simulation Before Construction

Contemporary Logic Design
Introduction


Debugging Skills:

- Improving the testability of the design
- Formulating a testing plan and choosing test cases
- Hypothesizing about the cause of the problem
- Isolating portions of the implementation for testing
- Effective use of laboratory instruments for troubleshooting


© R.H. Katz Transparency No. 1-12

Digital Systems

Digital vs. Analog Waveforms

 

Digital:
only assumes discrete values

 

Analog:
values vary over a broad range continuously

Advantages of Digital Systems

Analog systems: slight error in input yields large error in output

Digital systems more accurate and reliable

Readily available as self-contained, easy to cascade building blocks

Computers use digital circuits internally

Interface circuits (i.e., sensors & actuators) often analog

This course is about logic design, not system design (processor architecture), not circuit design (transistor level)

Digital Binary Systems

- **Two discrete values:**
yes, on, 5 volts, current flowing, magnetized North, "1"
no, off, 0 volts, no current flowing, magnetized South, "0"
- **Advantage of binary systems:**
rigorous mathematical foundation based on logic

IF the garage door is open
AND the car is running
THEN the car can be backed out of the garage

*both the door must
be open and the car
running before I can
back out*

IF N-S is green
AND E-W is red
AND 45 seconds has expired since the last light change
THEN we can advance to the next light configuration

the three preconditions must be true to imply the conclusion

Boolean Algebra and Logical Operators

Algebra: variables, values, operations

In Boolean algebra, the values are the symbols 0 and 1

If a logic statement is false, it has value 0

If a logic statement is true, it has value 1

Operations: AND, OR, NOT

X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1

X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1

X	NOT X
0	1
1	0

Hardware Systems and Logical Operators


IF the garage door is open
AND the car is running
THEN the car can be backed out of the garage

door open?	car running?	back out car?
false/0	false/0	false/0
false/0	true/1	false/0
true/1	false/0	false/0
true/1	true/1	TRUE/1

The Real World

Physical electronic components are continuous, not discrete!

 These are the building blocks of all digital components!



Transition from logic 1 to logic 0
does not take place instantaneously
in real digital systems

Intermediate values may be visible
for an instant

Boolean algebra useful for describing the steady state behavior of
digital systems

Be aware of the dynamic, time varying behavior too!

Digital Circuit Technologies

Integrated circuit technology
choice of conducting, non-conducting, sometimes conducting
("semiconductor") materials

whether or not their interaction allows electrons to flow forms
the basis for electrically controlled switches


Main technologies

MOS: Metal-Oxide-Silicon

Bipolar
Transistor-Transistor Logic
Emitter Coupled Logic

MOS Technology

Transistor
basic electrical switch

 


three terminal switch: gate, source, drain

voltage between gate and source exceeds threshold
switch is conducting or "closed"
electrons flow between source and drain

when voltage is removed,
the switch is "open" or non-conducting
connection between source and drain is broken

 Circuit that implements logical negation (NOT)




1 at input yields 0 at output
0 at input yields 1 at output

Inverter behavior as a function of input voltage
input ramps from 0V to 5V
output holds at 5V for some range of small input voltages
then changes rapidly, but not instantaneously!


remember distinction between
steady state and dynamic behavior

Combinational vs. Sequential Logic

 

Network implemented from switching elements or logic gates. The presence of feedback distinguishes between *sequential* and *combinational* networks.

 Combinational logic
no feedback among inputs and outputs
outputs are a pure function of the inputs
e.g., full adder circuit:
(A, B, Carry In) mapped into (Sum, Carry Out)



Sequential logic

inputs and outputs overlap
outputs depend on inputs *and* the entire history of execution!

network typically has only a limited number of unique configurations
these are called *states*
e.g., traffic light controller sequences infinitely through four states

new component in sequential logic networks:
storage elements to remember the current state

output and new state is a function of the inputs and the old state
i.e., the fed back inputs are the state!

Synchronous systems


period reference signal, the clock, causes the storage elements to accept new values and to change state

Asynchronous systems

no single indication of when to change state

Combinational vs Sequential Logic

Traffic Light Example

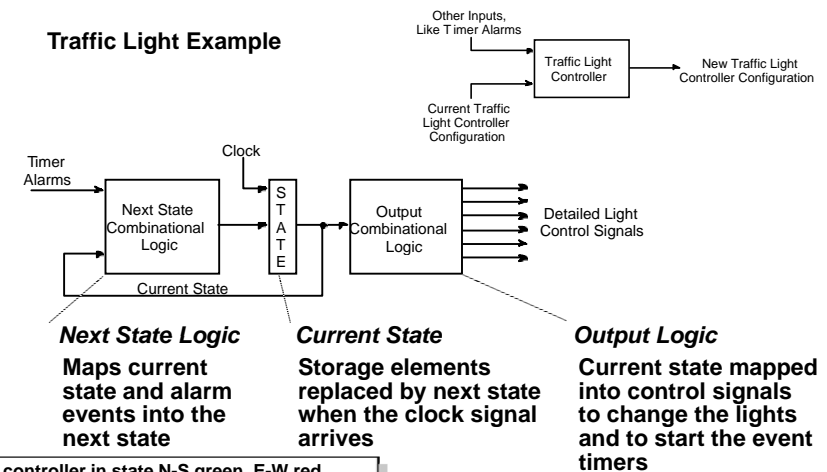

IF controller in state N-S green, E-W red
AND the 45 second timer alarm is asserted
THEN the next state becomes N-S yellow,
E-W red when the clk signal is next asserted

Representations of a Digital Design


Contemporary Logic Design
Introduction

Switches

A switch connects two points under control signal.

Normally Open when the control signal is 0 (false), the switch is open
when it is 1 (true), the switch is closed

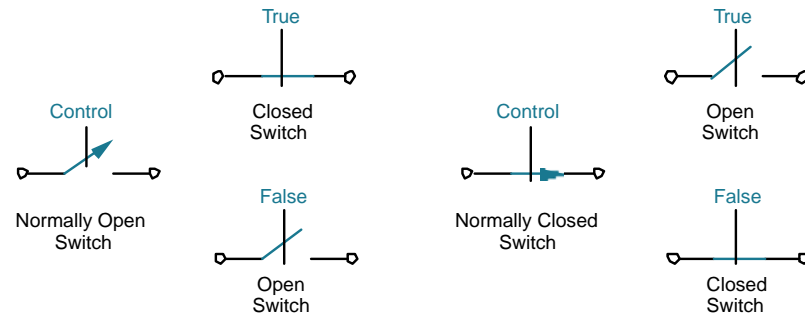Normally Closed when control is 1 (true), switch is open
when control is 0 (false), switch is closed



© R.H. Katz Transparency No. 1-25


Representations of a Digital Design: Switches

Contemporary Logic Design
Introduction

Examples: routing inputs to outputs through a maze

 
EXAMPLE:

IF car in garage
AND garage door open
AND car running
THEN back out car



 EXAMPLE:

IF car in driveway
OR (car in garage
AND NOT garage door
closed)
AND car running
THEN can back out car



Floating nodes:

what happens if the car is not running?
outputs are floating rather than forced to be false

Under all possible control signal settings


- (1) all outputs must be connected to some input through a path
- (2) no output is connected to more than one input through any path

© R.H. Katz Transparency No. 1-26


Representations of a Digital Design: Switches

Contemporary Logic Design
Introduction

 Implementation of AND and OR Functions with Switches



AND function
Series connection to TRUE

 

OR function
Parallel connection to TRUE

© R.H. Katz Transparency No. 1-27

Representations of a Digital Design

Contemporary Logic Design
Introduction

Truth Tables

tabulate all possible input combinations and their associated output values

Example: half adder
adds two binary digits
to form Sum and Carry

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

NOTE: 1 plus 1 is 0 with a carry of 1 in binary

Example: full adder
adds two binary digits and
Carry in to form Sum and
Carry Out

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

© R.H. Katz Transparency No. 1-28

Representations of a Digital Design

Contemporary Logic Design
Introduction

Boolean Algebra

values: 0, 1

variables: A, B, C, ..., X, Y, Z

operations: NOT, AND, OR, ...

NOT X is written as \bar{X}

X AND Y is written as $X \& Y$, or sometimes $X Y$

X OR Y is written as $X + Y$

Deriving Boolean equations from truth tables:

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Sum = $\bar{A} \bar{B} + A \bar{B} + A B \bar{Cin} + A B Cin$

OR'd together *product* terms for each truth table row where the function is 1

if input variable is 0, it appears in complemented form;
if 1, it appears uncomplemented

Carry = $A B$

© R.H. Katz Transparency No. 1-29

Representations of a Digital Design: Boolean Algebra

Contemporary Logic Design
Introduction

Another example:

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Sum = $\bar{A} \bar{B} Cin + \bar{A} B \bar{Cin} + A \bar{B} \bar{Cin} + A B Cin$

Cout = $\bar{A} B Cin + A \bar{B} Cin + A B \bar{Cin} + A B Cin$

© R.H. Katz Transparency No. 1-30

Representations of a Digital Design: Boolean Algebra

Contemporary Logic Design
Introduction

Reducing the complexity of Boolean equations

Laws of Boolean algebra can be applied to full adder's carry out function to derive the following simplified expression:

$$Cout = A Cin + B Cin + A B$$

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Verify equivalence with the original Carry Out truth table:

place a 1 in each truth table row where the product term is true

each product term in the above equation covers exactly two rows in the truth table; several rows are "covered" by more than one term

© R.H. Katz Transparency No. 1-31


Representations of a Digital Design

Contemporary Logic Design
Introduction


Gates

most widely used primitive building block in digital system design

Standard Logic Gate Representation

 

Half Adder Schematic

 

Net: electrically connected collection of wires


Netlist: tabulation of gate inputs & outputs and the nets they are connected to

© R.H. Katz Transparency No. 1-32

Representations of a Digital Design: Gates

Contemporary Logic Design
Introduction

Full Adder Schematic

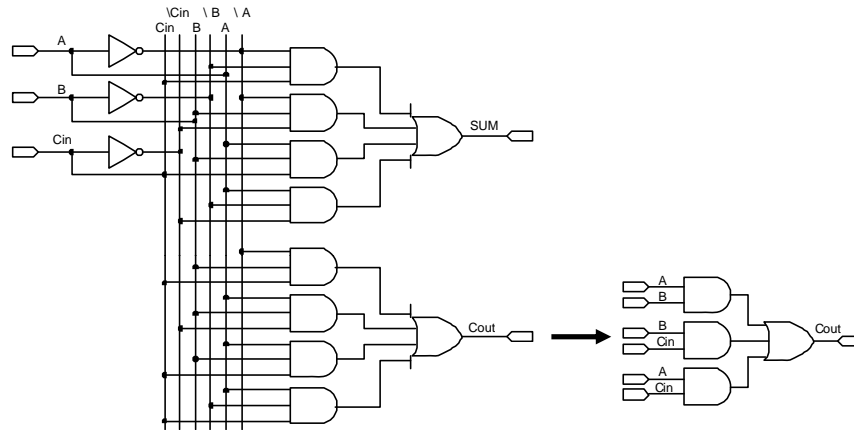

Fan-in: number of inputs to a gate

Fan-out: number of gate inputs an output is connected to

Technology "Rules of Composition" place limits on fan-in/fan-out

© R.H. Katz Transparency No. 1-33


Representations of a Digital Design

Contemporary Logic Design
Introduction

Waveforms

dynamic behavior of a circuit
real circuits have non-zero delays

Timing Diagram of the Half Adder

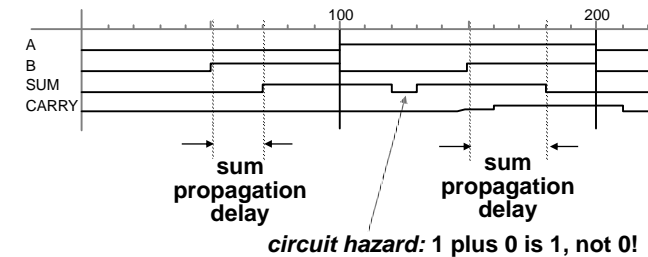

Output changes are delayed from input changes

The propagation delay is sensitive to paths in the circuit


Outputs may temporarily change from the correct value to the wrong value back again to the correct value: this is called a **glitch** or **hazard**

© R.H. Katz Transparency No. 1-34


Representations of a Digital Design: Waveforms

Contemporary Logic Design
Introduction


Tracing the Delays: A=0,B=0 to A=0,B=1

 


(i) Initial conditions

 

(ii) Y changes from 0 to 1

 

 (iii) Output of top AND gate changes after 10 time units



(iv) Output of OR gate changes after 10 time units

© R.H. Katz Transparency No. 1-35

Representations of a Digital Design

Contemporary Logic Design
Introduction


Blocks

structural organization of the design


black boxes with input and output connections

corresponds to well defined functions

 concentrates on how the components are composed by wiring



 Full Adder realized in terms of composition of half adder blocks



Block diagram representation of the Full Adder


© R.H. Katz Transparency No. 1-36

Representations of a Digital Design

Contemporary Logic Design
Introduction

Waveform Verification

 Does the composed full adder behave the same as the full gate implementation?



Sum, Cout waveforms lag input changes in time

How many time units after input change is it safe to examine the outputs?

© R.H. Katz Transparency No. 1-37

Representation of a Digital Design: Behaviors

Contemporary Logic Design
Introduction

ABEL Hardware Description Language

Truth Table Specification

```
MODULE half_adder;  
a, b, sum, carry PIN 1, 2, 3, 4;  
TRUTH_TABLE {[a, b] -> [sum, carry]}  
[0, 0] -> [0, 0];  
[0, 1] -> [1, 0];  
[1, 0] -> [1, 0];  
[1, 1] -> [0, 1];  
END half_adder;
```

Equation Specification

```
MODULE half_adder;  
a, b, sum, carry PIN 1, 2, 3, 4;  
EQUATIONS  
SUM = (A & !B) # (!A & B);  
CARRY = A & B;  
END half_adder;
```

AND OR NOT

© R.H. Katz Transparency No. 1-38

Representations of a Digital Design

Contemporary Logic Design
Introduction

Behaviors

Hardware description languages
structure and function of the digital design

Example: Half Adder in VHDL

```
-- ***** inverter gate model *****  
-- external ports  
ENTITY inverter_gate;  
  PORT (a: IN BIT; z: OUT BIT);  
END inverter_gate;
```

Black Box View
as seen by outside
world

```
-- internal behavior  
ARCHITECTURE behavioral OF inverter_gate IS  
BEGIN  
  z <= NOT a AFTER 10 ns;  
END behavioral;
```

Internal Behavior
Note delay statement

```
-- ***** and gate model *****  
-- external ports  
ENTITY and_gate;  
  PORT (a, b: IN BIT; z: OUT BIT);  
END and_gate;
```

```
-- internal behavior  
ARCHITECTURE behavioral OF and_gate IS  
BEGIN  
  z <= a AND b AFTER 10 ns;  
END behavioral;
```

© R.H. Katz Transparency No. 1-39

Representation of a Digital Design: Behaviors

Contemporary Logic Design
Introduction

```
-- ***** or gate model *****  
-- external ports  
ENTITY or_gate;  
  PORT (a, b: IN BIT; z: OUT BIT);  
END or_gate;
```

AND, OR, NOT models
typically included in a
library

```
-- internal behavior  
ARCHITECTURE behavioral OF or_gate IS  
BEGIN  
  z <= a OR b AFTER 10 ns;  
END behavioral;
```

```
-- ***** half adder model *****  
-- external ports  
ENTITY half_adder;  
  PORT (a_in, b_in: INPUT; sum, c_out: OUTPUT);  
END half_adder;
```

```
-- internal structure  
ARCHITECTURE structural OF half_adder IS  
  -- component types to use  
  COMPONENT inverter_gate  
    PORT (a: IN BIT; z: OUT BIT); END COMPONENT;  
  COMPONENT and_gate  
    PORT (a, b: IN BIT; z: OUT BIT); END COMPONENT;  
  COMPONENT or_gate  
    PORT (a, b: IN BIT; z: OUT BIT); END COMPONENT;
```

Particular components
to be used within the
model of the half adder

```
-- internal signal wires  
SIGNAL s1, s2, s3, s4: BIT;
```

© R.H. Katz Transparency No. 1-40

Representation of a Digital Design: Behaviors


Contemporary Logic Design
Introduction

BEGIN

```
-- one line for each gate, describing its type and connections  
i1: inverter_gate PORT MAP (a_in, s1);  
i2: inverter_gate PORT MAP (b_in, s2);  
a1: and_gate PORT MAP (b_in, s1, s3);  
a2: and_gate PORT MAP (a_in, s2, s4);  
o1: or_gate PORT MAP (s3, s4, sum);  
END structural;
```

Textual description
of the netlist

 This VHDL specification corresponds to the following labeled schematic



© R.H. Katz Transparency No. 1-41

Rapid Electronic System Prototyping

Contemporary Logic Design
Introduction

Goals:

- quick construction of digital systems to prove concept
- rapid exploration of alternative design approaches
- performance traded off for faster path to implementation

Techniques:

- computer-aided design tools
 - simulation: find out how the design will behave before constructing it
 - synthesis: generate detailed descriptions, like schematics, from high level descriptions, like Boolean equations
- quick turnaround implementation technologies
- programmable logic

© R.H. Katz Transparency No. 1-42


Rapid Electronic System Prototyping:

Contemporary Logic Design
Introduction

Computer-Aided Design

Synthesis tools

 - create a portion of the design from other portions
- map more abstract representation to more physical representation



map a representation into a more optimized form of that representation, e.g., espresso

© R.H. Katz Transparency No. 1-43

Rapid Electronic System Prototyping

Contemporary Logic Design
Introduction

Simulation

- program which dynamically executes an abstract design description
- obtain verification of functional correctness and some timing information before the design is physically constructed
- easier to probe and debug a simulation than an implemented design
- simulation cannot guarantee that a design will work
 - only as good as the test cases attempted
 - does not check electrical errors
 - abstracts away some of the realities of a real system

Logic Simulation

- design described in terms of logic gates
- values are 0, 1 (plus others to be introduced)
- good for truth table verification

Timing Simulation

- waveform inputs and outputs
- model of gate delays
- are the waveform shapes what was expected?
- identification of performance bottlenecks

© R.H. Katz Transparency No. 1-44

Rapid Electronic System Implementation

Contemporary Logic Design
Introduction

Rapid Implementation Technologies

the function and interconnect of a component can be "personalized"

alternative to discrete logic gates and wires

reduces wiring complexity and parts count

facilitates more rapid design changes and enhancements

Programming with 1's and 0's

component function configured through truth table

interconnect among internal modules also configured in this way
selectively blown fuses
programmable switching matrix configured by 1's and 0's

© R.H. Katz Transparency No. 1-45

Rapid Electronic System Prototyping

Contemporary Logic Design
Introduction

Example: Read-Only Memories


hardware implementation of a two dimensional array

inputs form the index into the array


the binary word at the indexed memory location contains the
output values

contents are programmed once, read many times

Half Adder Realized as a ROM:

 

Full Adder Realized as a ROM:

 

© R.H. Katz Transparency No. 1-46

Chapter Review

Contemporary Logic Design
Introduction

We have introduced:

- *the process of design:*
 - functional decomposition and design by assembly
- *the kinds of systems we will be designing:*
 - combinational and sequential logic
 - binary digital systems
 - implemented in MOS and bipolar technology
- *the many levels of design representation:*
 - from switches to behavioral descriptions
- *the changing technological landscape:*
 - rapid electronic system implementation
 - facilitated by computer-aided design tools
 - (in particular, synthesis and simulation tools)
 - and programmable logic devices

© R.H. Katz Transparency No. 1-47