

Chapter # 4: Programmable and Steering Logic

Contemporary Logic Design

Randy H. Katz
University of California, Berkeley

June 1993


Chapter Overview

- *PALs and PLAs*
- *Non-Gate Logic*
Switch Logic
Multiplexers/Selectors and Decoders
Tri-State Gates/Open Collector Gates
ROM
- *Combinational Logic Design Problems*
Seven Segment Display Decoder
Process Line Controller
Logical Function Unit
Barrel Shifter

PALs and PLAs

Pre-fabricated building block of many AND/OR gates (or NOR, NAND)
"Personalized" by making or breaking connections among the gates

 Programmable Array Block Diagram for Sum of Products Form



PALs and PLAs

Key to Success: Shared Product Terms

Equations

Example:

$$\begin{aligned} F_0 &= A + B' C' \\ F_1 &= A C' + A B \\ F_2 &= B' C' + A B \\ F_3 &= B' C + A \end{aligned}$$

Product term	Inputs			Outputs			
	A	B	C	F ₀	F ₁	F ₂	F ₃
AB	1	1	-	0	⊕	⊕	0
$\overline{B}C$	-	0	1	0	0	0	1
$\overline{A}C$	1	-	0	0	1	0	0
$\overline{B}C$	-	0	0	⊕	0	⊕	0
A	1	-	-	⊕	0	0	⊕

Input Side:

1 = asserted in term
0 = negated in term
- = does not participate

Output Side:


1 = term connected to output
0 = no connection to output

Reuse of terms

PALs and PLAs

Contemporary Logic Design
Prog. & Steering Logic

Example Continued

 


© R.H. Katz Transparency No. 4-5

PALs and PLAs

Contemporary Logic Design
Prog. & Steering Logic

Example Continued

 


Note: some array structures work by making connections rather than breaking them

© R.H. Katz Transparency No. 4-6


PALs and PLAs

Contemporary Logic Design
Prog. & Steering Logic

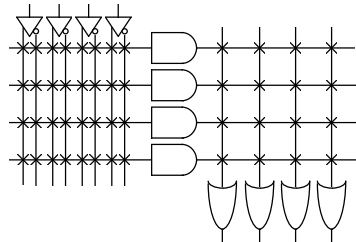Alternative representation for high fan-in structures



 Short-hand notation so we don't have to draw all the wires!



Notation for implementing
 $F0 = AB + \bar{A}B$
 $F1 = C\bar{D} + \bar{C}D$

© R.H. Katz Transparency No. 4-7

PALs and PLAs

Contemporary Logic Design
Prog. & Steering Logic

Design Example

Multiple functions of A, B, C

$$F1 = ABC$$


$$F2 = A + B + C$$

$$F3 = \overline{ABC}$$

$$F4 = A + B + C$$

$$F5 = A \text{ xor } B \text{ xor } C$$
 
$$F6 = A \text{ xnor } B \text{ xnor } C$$




© R.H. Katz Transparency No. 4-8

PALs and PLAs

What is difference between Programmable Array Logic (PAL) and Programmable Logic Array (PLA)?

 PAL concept — implemented by Monolithic Memories
constrained topology of the OR Array



A given column of the OR array
has access to only a subset of
the possible product terms

PLA concept — generalized topologies in AND and OR planes


PALs and PLAs

Design Example: BCD to Gray Code Converter


Truth Table

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	0
0	1	1	0	1	0	1	1
0	1	1	1	1	0	0	1
1	0	0	0	1	0	0	1
1	0	0	1	1	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X


K-maps

 


K-map for W

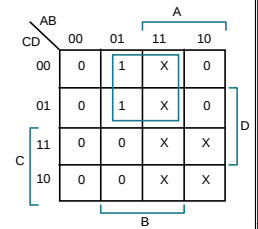

K-map for X

 

K-map for Y

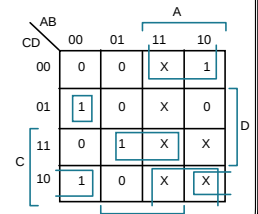

K-map for Z

Minimized Functions:

$$W = A + B D + B C$$


$$X = B C'$$

$$Y = B + C$$

$$Z = A'B'C'D + B C D + A D' + B' C D'$$

PALs and PLAs


Programmed PAL:

 

4 product terms per each OR gate

PALs and PLAs

 Code Converter Discrete Gate Implementation




- 1: 7404 hex inverters
- 2,5: 7400 quad 2-input NAND
- 3: 7410 tri 3-input NAND
- 4: 7420 dual 4-input NAND

4 SSI Packages vs. 1 PLA/PAL Package!

PALs and PLAs

Contemporary Logic Design
Prog. & Steering Logic

Another Example: Magnitude Comparator

 

© R.H. Katz Transparency No. 4-13

Non-Gate Logic

Contemporary Logic Design
Prog. & Steering Logic

Introduction

AND-OR-Invert
PAL/PLA

Generalized Building Blocks
Beyond Simple Gates

Kinds of "Non-gate logic":


- switching circuits built from CMOS transmission gates
- multiplexer/selecter functions
- decoders
- tri-state and open collector gates
- read-only memories

© R.H. Katz Transparency No. 4-14

Steering Logic: Switches

Contemporary Logic Design
Prog. & Steering Logic

Voltage Controlled Switches

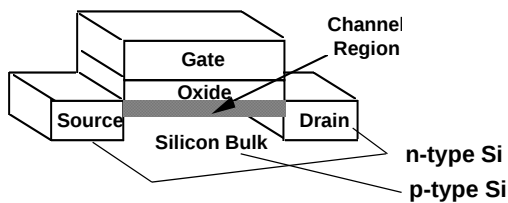

"n-Channel MOS"

Metal Gate, Oxide, Silicon Sandwich

Diffusion regions: negatively charged ions driven into Si surface

Si Bulk: positively charged ions


By "pulling" electrons to the surface, a conducting channel is formed

© R.H. Katz Transparency No. 4-15


Steering Logic

Contemporary Logic Design
Prog. & Steering Logic

Voltage Controlled Switches

 

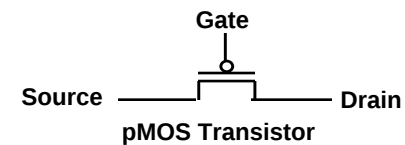Logic 1 on gate,
Source and Drain connected




Logic 0 on gate,
Source and Drain connected

© R.H. Katz Transparency No. 4-16

Steering Logic

Logic Gates from Switches

 


Pull-up network constructed from pMOS transistors

Pull-down network constructed from nMOS transistors

Steering Logic

Inverter Operation

 


Input is 1
Pull-up does not conduct
Pull-down conducts
Output connected to GND

Input is 0
Pull-up conducts
Pull-down does not conduct
Output connected to VDD

Steering Logic

NAND Gate Operation

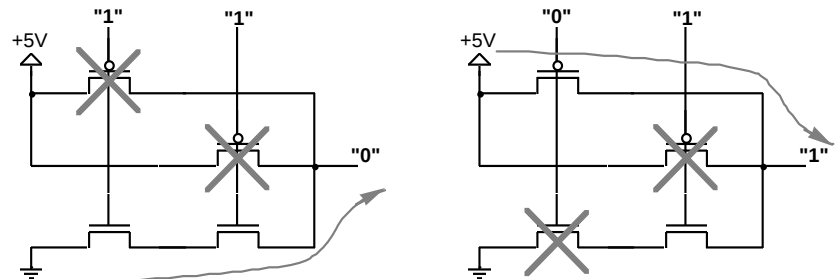


A = 1, B = 1
Pull-up network does not conduct
Pull-down network conducts
Output node connected to GND

A = 0, B = 1
Pull-up network has path to VDD
Pull-down network path broken
Output node connected to VDD

Steering Logic

NOR Gate Operation

 

A = 0, B = 0
Pull-up network conducts
Pull-down network broken
Output node at VDD

A = 1, B = 0
Pull-up network broken
Pull-down network conducts
Output node at GND

Steering Logic


Contemporary Logic Design
Prog. & Steering Logic

CMOS Transmission Gate

nMOS transistors good at passing 0's but bad at passing 1's

pMOS transistors good at passing 1's but bad at passing 0's

 perfect "transmission" gate places these in parallel:




© R.H. Katz Transparency No. 4-21

Steering Logic


Contemporary Logic Design
Prog. & Steering Logic

Selection Function/Demultiplexer Function with Transmission Gates

 Selector:
Choose I0 if S = 0
Choose I1 if S = 1



 Demultiplexer:
I to Z0 if S = 0
I to Z1 if S = 1




© R.H. Katz Transparency No. 4-22

Steering Logic

Contemporary Logic Design
Prog. & Steering Logic

 Use of Multiplexer/Demultiplexer in Digital Systems



So far, we've only seen point-to-point connections among gates

Mux/Demux used to implement multiple source/multiple destination interconnect


© R.H. Katz Transparency No. 4-23

Steering Logic

Contemporary Logic Design
Prog. & Steering Logic

Well-formed Switching Networks

 Problem with the Demux implementation:
multiple outputs, but only one connected to the input!



The fix: additional logic to drive every output to a known value


Never allow outputs to "float"

© R.H. Katz Transparency No. 4-24

Steering Logic

Complex Steering Logic Example

 
N Input Tally Circuit: count # of 1's in the inputs



Steering Logic

Complex Steering Logic Example

Operation of the 1 Input Tally Circuit

 


Input is 0, straight through switches enabled

Steering Logic

Complex Steering Logic Example

Operation of 1 input Tally Circuit

 


Input = 1, diagonal switches enabled

Steering Logic

Complex Steering Logic Example

Extension to the 2-input case

 


Conventional logic implementation

Steering Logic

Contemporary Logic Design
Prog. & Steering Logic

Complex Steering Logic Example

 Switch Logic Implementation: 2-input Tally Circuit



Cascade the 1-input implementation!


© R.H. Katz Transparency No. 4-29

Steering Logic

Contemporary Logic Design
Prog. & Steering Logic

Complex Steering Logic Example

Operation of 2-input implementation

 


© R.H. Katz Transparency No. 4-30

Multiplexers/Selectors

Contemporary Logic Design
Prog. & Steering Logic

Use of Multiplexers/Selectors

Multi-point connections

 

Multiple input sources

Multiple output destinations

© R.H. Katz Transparency No. 4-31

Multiplexers/Selectors

Contemporary Logic Design
Prog. & Steering Logic

General Concept

2^n data inputs, n control inputs, 1 output

used to connect 2^n points to a single point

control signal pattern form binary index of input connected to output

$$Z = A' I_0 + A I_1$$

A	Z
0	I_0
1	I_1

Functional form

Logical form


I_1	I_0	A	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Two alternative forms
for a 2:1 Mux Truth Table


© R.H. Katz Transparency No. 4-32

Multiplexers/Selectors

 
Contemporary Logic Design
Prog. & Steering Logic



$$Z = A' I_0 + A I_1$$

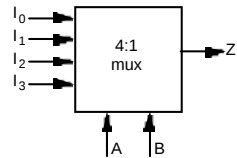
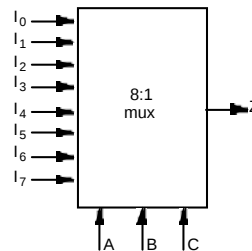
$$Z = A' B' I_0 + A' B I_1 + A B' I_2 + A B I_3$$



$$Z = A' B' C' I_0 + A' B' C I_1 + A' B C' I_2 + A' B C I_3 + A B' C' I_4 + A B' C I_5 + A B C' I_6 + A B C I_7$$


In general, $Z = \sum_{k=0}^{2^n-1} m_k I_k$
in minterm shorthand form for a $2^n:1$ Mux

© R.H. Katz Transparency No. 4-33

Multiplexers/Selectors


Contemporary Logic Design
Prog. & Steering Logic

Alternative Implementations

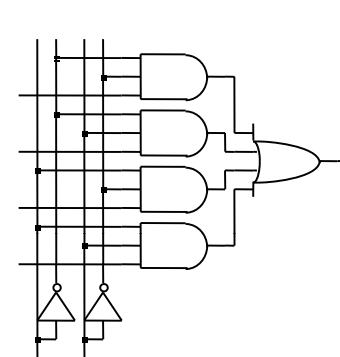

Gate Level
Implementation
of 4:1 Mux

thirty six transistors

 

Transmission Gate
Implementation
of 4:1 Mux


twenty transistors

© R.H. Katz Transparency No. 4-34

Multiplexer/Selector

Contemporary Logic Design
Prog. & Steering Logic


Large multiplexers can be implemented by cascaded smaller ones

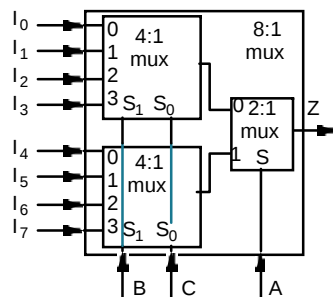

Alternative 8:1 Mux Implementation

Control signals B and C simultaneously
choose one of I0-I3 and I4-I7

 Control signal A chooses which of the
upper or lower MUX's output to gate to Z



© R.H. Katz Transparency No. 4-35

Multiplexer/Selector

Contemporary Logic Design
Prog. & Steering Logic

Multiplexers/selectors as a general purpose logic block

$2^{n-1}:1$ multiplexer can implement any function of n variables


n-1 control variables; remaining variable is a data input to the mux

Example:

$$F(A,B,C) = m_0 + m_2 + m_6 + m_7$$


$$= A' B' C' + A' B C' + A B C' + A B C$$
 
$$= A' B' (C') + A' B (C') + A B' (0) + A B (1)$$



"Lookup Table"


A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

© R.H. Katz Transparency No. 4-36


Multiplexer/Selector

Generalization

 

 Example:

G(A,B,C,D) can be implemented by an 8:1 MUX:



Decoders/Demultiplexers

Decoder: single data input, n control inputs, 2^n outputs

control inputs (called select S) represent Binary index of output to which the input is connected

data input usually called "enable" (G)

1:2 Decoder:

$$O0 = G \cdot \overline{S}; \quad O1 = G \cdot S$$

2:4 Decoder:

$$O0 = G \cdot \overline{S0} \cdot \overline{S1}$$

$$O1 = G \cdot \overline{S0} \cdot S1$$

$$O2 = G \cdot S0 \cdot \overline{S1}$$

$$O3 = G \cdot S0 \cdot S1$$

3:8 Decoder:

$$O0 = G \cdot \overline{S0} \cdot \overline{S1} \cdot \overline{S2}$$

$$O1 = G \cdot \overline{S0} \cdot \overline{S1} \cdot S2$$

$$O2 = G \cdot \overline{S0} \cdot S1 \cdot \overline{S2}$$

$$O3 = G \cdot \overline{S0} \cdot S1 \cdot S2$$

$$O4 = G \cdot S0 \cdot \overline{S1} \cdot \overline{S2}$$


$$O5 = G \cdot S0 \cdot \overline{S1} \cdot S2$$

$$O6 = G \cdot S0 \cdot S1 \cdot \overline{S2}$$

$$O7 = G \cdot S0 \cdot S1 \cdot S2$$



Decoders/Demultiplexers

Alternative Implementations

 

Decoders/Demultiplexers


Switch Logic Implementations

  

Correct 1:2 Decoder Implementation

Decoders/Demultiplexers

Switch Implementation of 2:4 Decoder

 

Operation of 2:4 Decoder


$S_0 = 0, S_1 = 0$

one straight thru path

three diagonal paths

Decoder/Demultiplexer

Decoder as a Logic Building Block

 

Decoder Generates Appropriate
Minterm based on Control Signals

Example Function:


$$F_1 = A'BC'D + A'B'CD + ABCD$$

$$F_2 = ABC'D' + ABC$$

$$F_3 = (A' + B' + C' + D')$$

Decoder/Demultiplexer

Decoder as a Logic Building Block

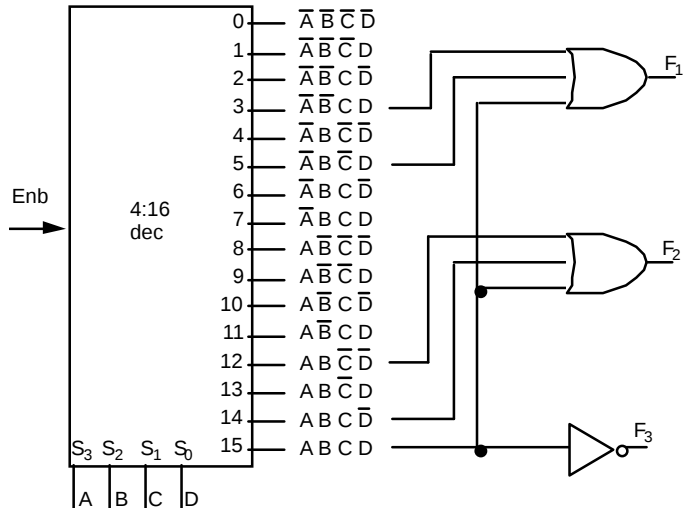


If active low enable, then use NAND gates!

Multiplexers/Decoders

Alternative Implementations of 32:1 Mux

Multiplexer Only

 


Multiplexers/Decoders

Contemporary Logic Design
Prog. & Steering Logic

Alternative Implementations of 32:1 Mux

Multiplexer + Decoder


 


© R.H. Katz Transparency No. 4-45

Multiplexers/Decoders

Contemporary Logic Design
Prog. & Steering Logic

5:32 Decoder

  

© R.H. Katz Transparency No. 4-46

Tri-State and Open-Collector

Contemporary Logic Design
Prog. & Steering Logic

The Third State

Logic States: "0", "1"

Don't Care/Don't Know State: "X" (must be some value in real circuit!)

Third State: "Z" — high impedance — infinite resistance, no connection

Tri-state gates: output values are "0", "1", and "Z"
additional input: output enable (OE)


A	OE	F
X	0	Z
0	1	0
1	1	1

When OE is high, this gate is a non-inverting "buffer"

When $\overline{OE}$ is low, it is as though the gate was disconnected from the output!

This allows more than one gate to be connected to the same output wire, as long as only one has its output enabled at the same time

Non-inverting buffer's timing waveform

 


© R.H. Katz Transparency No. 4-47

Tri-state and Open Collector

Contemporary Logic Design
Prog. & Steering Logic

 Using tri-state gates to implement an economical multiplexer:



When SelectInput is asserted high
Input1 is connected to F


When SelectInput is driven low
Input0 is connected to F

This is essentially a 2:1 Mux

© R.H. Katz Transparency No. 4-48


Tri-State and Open Collector

Alternative Tri-state Fragment

 

Tri-State and Open Collector

4:1 Multiplexer, Revisited

 

Decoder + 4 tri-state Gates


Tri-State and Open Collector

Open Collector

another way to connect multiple gates to the same output wire


gate only has the ability to pull its output low; it cannot actively drive the wire high

 this is done by pulling the wire up to a logic 1 voltage through a resistor



Tri-State and Open Collector

4:1 Multiplexer

 

Decoder + 4 Open Collector Gates


Read-Only Memories

ROM: Two dimensional array of 1's and 0's

Row is called a "word"; index is called an "address"

Width of row is called *bit-width* or *wordsize*

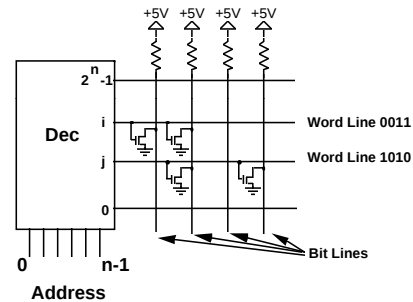Address is input, selected word is output



Internal Organization

Read-Only Memories


Example: Combination Logic Implementation

$$F_0 = A' B' C + A B' C' + A B' C$$

$$F_1 = A' B' C + A' B C' + A B C$$


$$F_2 = A' B' C' + A' B' C + A B' C'$$

$$F_3 = A' B C + A B' C' + A B C'$$

 

Read-Only Memories

 Not unlike a PLA structure with a fully decoded AND array!



ROM vs. PLA:

ROM approach advantageous when

- (1) design time is short (no need to minimize output functions)
- (2) most input combinations are needed (e.g., code converters)
- (3) little sharing of product terms among output functions

ROM problem: size doubles for each additional input, can't use don't cares



PLA approach advantageous when

- (1) design tool like espresso is available
- (2) there are relatively few unique minterm combinations
- (3) many minterms are shared among the output functions

PAL problem: constrained fan-ins on OR planes

Read-Only Memories

2764 EPROM
8K x 8

  

16K x 16
Subsystem

Combinational Logic Word Problems

Contemporary Logic Design
Prog. & Steering Logic

General Design Procedure

1. Understand the Problem
what is the circuit supposed to do?
write down inputs (data, control) and outputs
draw block diagram or other picture
2. Formulate the Problem in terms of a truth table or other suitable design representation
truth table or waveform diagram
3. Choose Implementation Target
ROM, PAL, PLA, Mux, Decoder + OR, Discrete Gates
4. Follow Implementation Procedure
K-maps, espresso, misII

© R.H. Katz Transparency No. 4-57

Combinational Logic Word Problems

Contemporary Logic Design
Prog. & Steering Logic

Process Line Control Problem

Statement of the Problem

Rods of varying length (+/-10%) travel on conveyor belt
Mechanical arm pushes rods within spec (+/-5%) to one side
Second arm pushes rods too long to other side
Rods too short stay on belt

3 light barriers (light source + photocell) as sensors

Design combinational logic to activate the arms

Understanding the Problem

Inputs are three sensors, outputs are two arm control signals

Assume sensor reads "1" when tripped, "0" otherwise

Call sensors A, B, C


Draw a picture!

© R.H. Katz Transparency No. 4-58

Combinational Logic Word Problems

Contemporary Logic Design
Prog. & Steering Logic

Process Control Problem

 

Where to place the light sensors A, B, and C to distinguish among the three cases?


Assume that A detects the leading edge of the rod on the conveyor

© R.H. Katz Transparency No. 4-59

Combinational Logic Word Problems

Contemporary Logic Design
Prog. & Steering Logic

Process Control Problem

 

A to B distance place apart at specification - 5%

A to C distance placed apart at specification +5%

© R.H. Katz Transparency No. 4-60

Combinational Logic Word Problems

Contemporary Logic Design
Prog. & Steering Logic

Process Control Problem

A	B	C	Function
0	0	0	X
0	0	1	X
0	1	0	X
0	1	1	X
1	0	0	too short
1	0	1	X
1	1	0	in spec
1	1	1	too long

Truth table and logic implementation
now straightforward

"too long" = $A B C$
(all three sensors tripped)

"in spec" = $A B C'$
(first two sensors tripped)

© R.H. Katz Transparency No. 4-61

Combinational Logic Word Problems

Contemporary Logic Design
Prog. & Steering Logic

BCD to 7 Segment Display Controller



Understanding the problem:

input is a 4 bit bcd digit

output is the control signals for the display

4 inputs A, B, C, D

7 outputs C0 — C6

  

Block Diagram

© R.H. Katz Transparency No. 4-62

Combinational Logic Word Problems

Contemporary Logic Design
Prog. & Steering Logic

BCD to 7 Segment Display Controller

D	
0	
1	
0	
1	
0	
1	
0	
1	
0	
1	
0	
1	

Formulate the problem in terms of a
truth table

Choose implementation target:

if ROM, we are done

don't cares imply PAL/PLA may be
attractive

Follow implementation procedure:

hand reduced K-maps

vs.


espresso

© R.H. Katz Transparency No. 4-63

Combinational Logic Word Problems

Contemporary Logic Design
Prog. & Steering Logic

BCD to 7 Segment Display Controller

 

$$\begin{aligned} C0 &= A + B D + C + B' D' \\ C1 &= A + C' D' + C D + B' \\ C2 &= A + B + C' + D \end{aligned}$$

14 Unique Product Terms


$$\begin{aligned} C3 &= B' D' + C D' + B C' D + B' C \\ C4 &= B' D' + C D \\ C5 &= A + C' D' + B D' + B' C' \\ C6 &= A + C D' + B C' + B' C \end{aligned}$$

© R.H. Katz Transparency No. 4-64

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

16H8PAL
Can Implement
the function

 


Note: Fuse number = first fuse number + increment

© R.H. Katz Transparency No. 4-65

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

14H8PAL
Cannot Implement
the function

 

Note: Fuse number = first fuse number + increment

© R.H. Katz Transparency No. 4-66

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

```
.i 4
.o 7
.ilb a b c d
.ob c0 c1 c2 c3 c4 c5 c6
.p 16
0000 1111110
0001 0110000
0010 1101101
0011 1111001
0100 0110011
0101 1011011
0110 1011111
0111 1110000
1000 1111111
1001 1110011
1010 -----
1011 -----
1100 -----
1101 -----
1110 -----
1111 -----
.e
```

espresso
output

$C0 = B' C' D + C D + B' D' + B C D' + A$
 $C1 = B' D + C' D' + C D + B' D'$
 $C2 = B' D + B C' D + C' D' + C D + B C D'$
 $C3 = B' C' D + B' D + B' D' + B C D'$
 $C4 = B' D' + B C D'$
 $C5 = B' C' D + C' D' + A + B C D'$
 $C6 = B' C + B C' + B C D' + A$

9 Unique Product Terms!

63 Literals, 20 Gates


espresso
input

© R.H. Katz Transparency No. 4-67

Combinational Logic Word Problems

BCD to 7 Segment Display Controller

PLA Implementation

 

© R.H. Katz Transparency No. 4-68

Combinational Logic Word Problems

Logical Function Unit

Statement of the Problem:

C	C	C2	F	Comments
1	1	0	1	always 1
1	1	1	A + B	logical or
1	1	0	$\overline{A+B}$	logical nand
1	1	1	A xor B	logical xor
1	1	0	A xnor B	logical xnor
1	1	1	A*B	logical and
1	1	0	$\overline{A*B}$	logical nor
1	1	1	0	always 0

3 control inputs: C0, C1, C2
2 data inputs: A, B
1 output: F

52 literals

33 gates

Ineffective use of don't cares

Combinational Logic Word Problems

Logical Function Unit

Follow implementation procedure

$$F = C2' A' B' + C0' A B' + C0' A' B + C1' A B$$

5 gates, 5 inverters

Also four packages:
4 x 3-input NAND
1 x 4-input NAND

**Alternative: 32 x 1-bit ROM
single package**



Combinational Logic Word Problems

Contemporary Logic Design
Prog. & Steering Logic


8-Input Barrel Shifter

Specification:

Inputs: D7, D6, ..., D0
Outputs: O7, O6, ..., O0
Control: S2, S1, S0

shift input the specified number of positions to the right

Understand the problem:

 

© R.H. Katz Transparency No. 4-73

Combinational Logic Word Problems

Contemporary Logic Design
Prog. & Steering Logic

8-Input Barrel Shifter

Function Table

S2	S1	S0	O7	O6	O5	O4	O3	O2	O1	O0
0	0	0	D7	D6	D5	D4	D3	D2	D1	D0
0	0	1	D6	D5	D4	D3	D2	D1	D0	D7
0	1	0	D5	D4	D3	D2	D1	D0	D7	D6
0	1	1	D4	D3	D2	D1	D0	D7	D6	D5
1	0	0	D3	D2	D1	D0	D7	D6	D5	D4
1	0	1	D2	D1	D0	D7	D6	D5	D4	D3
1	1	0	D1	D0	D7	D6	D5	D4	D3	D2
1	1	1	D0	D7	D6	D5	D4	D3	D2	D1

Boolean equations

$$\begin{aligned}
 O7 &= S2' S1' S0' D7 + S2' S1' S0 D6 + \dots + S2 S1 S0 D0 \\
 O6 &= S2' S1' S0' D6 + S2' S1' S0 D5 + \dots + S2 S1 S0 D7 \\
 O5 &= S2' S1' S0' D5 + S2' S1' S0 D4 + \dots + S2 S1 S0 D6 \\
 O4 &= S2' S1' S0' D4 + S2' S1' S0 D3 + \dots + S2 S1 S0 D5 \\
 O3 &= S2' S1' S0' D3 + S2' S1' S0 D2 + \dots + S2 S1 S0 D4 \\
 O2 &= S2' S1' S0' D2 + S2' S1' S0 D1 + \dots + S2 S1 S0 D3 \\
 O1 &= S2' S1' S0' D1 + S2' S1' S0 D0 + \dots + S2 S1 S0 D2 \\
 O0 &= S2' S1' S0' D0 + S2' S1' S0 D7 + \dots + S2 S1 S0 D1
 \end{aligned}$$

© R.H. Katz Transparency No. 4-74

Combinational Logic Word Problems


Contemporary Logic Design
Prog. & Steering Logic

8-Input Barrel Shifter

Straightforward gate logic implementation OR

8 by 8:1 multiplexer (wiring mess!) OR

Switch logic

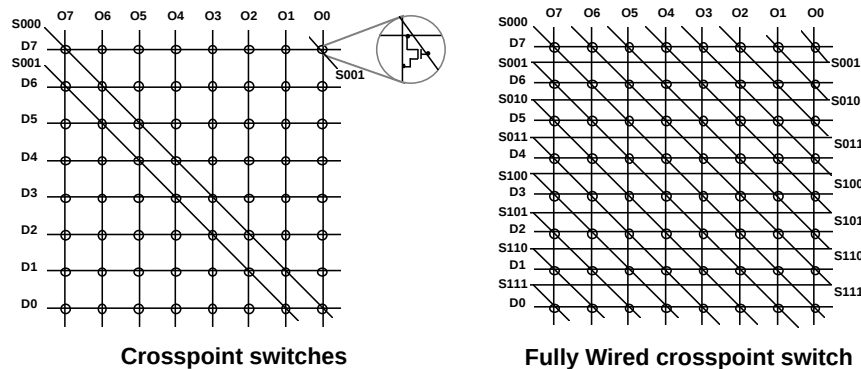

© R.H. Katz Transparency No. 4-75

Chapter Review

Contemporary Logic Design
Prog. & Steering Logic

• Non-Simple Gate Logic Building Blocks:

PALs/PLAs

Multiplexers/Selectors

Decoders

ROMs

Tri-state, Open Collector

• Combinational Word Problems:

Understand the Problem

Formulate in terms of a Truth Table

Choose implementation technology

Implement by following the design procedure

© R.H. Katz Transparency No. 4-76