

## Chapter #6: Sequential Logic Design

*Contemporary Logic Design*


Randy H. Katz  
University of California, Berkeley

June 1993


### Chapter Overview

- **Sequential Networks**  
Simple Circuits with Feedback  
R-S Latch  
J-K Flipflop  
Edge-Triggered Flipflops
- **Timing Methodologies**  
Cascading Flipflops for Proper Operation  
Narrow Width Clocking vs. Multiphase Clocking  
Clock Skew
- **Realizing Circuits with Flipflops**  
Choosing a FF Type  
Characteristic Equations  
Conversion Among Types
- **Metastability and Asynchronous Inputs**
- **Self-Timed Circuits**

### Sequential Switching Networks

 

 Circuits with Feedback:  
Some outputs are also inputs



Traffic Light Controller is a complex  
sequential logic network

Sequential logic forms basis for building  
"memory" into circuits

These memory elements are primitive  
sequential circuits

### Sequential Switching Networks


#### **Simple Circuits with Feedback**

Primitive memory elements created from cascaded gates


Simplest gate component: inverter

Basis for commercial static RAM designs

 Cross-coupled NOR gates and NAND gates also possible



Cascaded Inverters: Static Memory Cell

 


Selectively break feedback path to load new  
value into cell

## Sequential Switching Networks


Contemporary Logic Design  
Sequential Logic

### Inverter Chains

 

Odd # of stages leads to ring oscillator  
Snapshot taken just before last inverter changes  
Output high propagating thru this stage

### Timing Waveform:

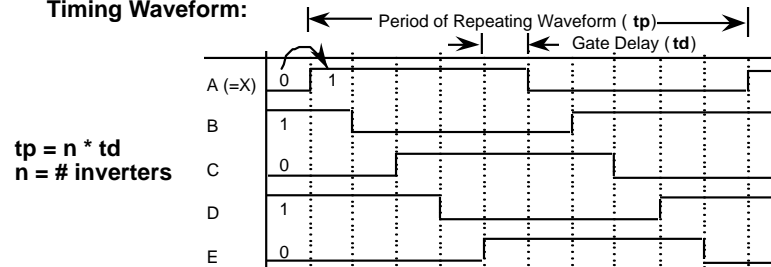


© R.H. Katz Transparency No. 6-5

## Sequential Switching Networks

Contemporary Logic Design  
Sequential Logic

### Inverter Chains

 


Propagation of Signals through the Inverter Chain

© R.H. Katz Transparency No. 6-6


## Sequential Switching Networks

Contemporary Logic Design  
Sequential Logic


### Cross-Coupled NOR Gates

 

 Just like cascaded inverters,  
with capability to force output  
to 0 (reset) or 1 (set)



### Timing Waveform

 

© R.H. Katz Transparency No. 6-7

## Sequential Switching Networks

Contemporary Logic Design  
Sequential Logic

### State Behavior of R-S Latch

S	R	Q
0	0	hold
0	1	0
1	0	1
1	1	unstable




Truth Table Summary  
of R-S Latch Behavior




© R.H. Katz Transparency No. 6-8
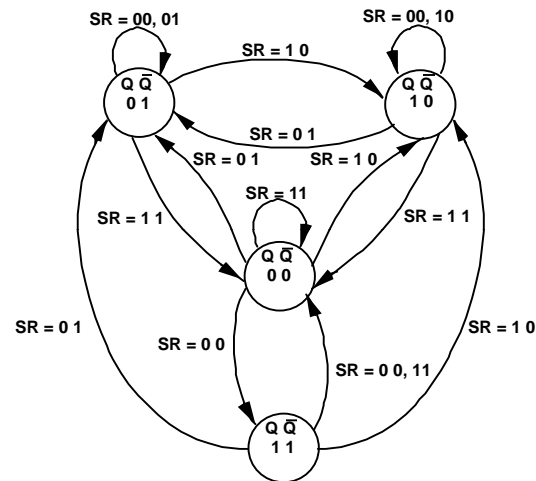
### ***Theoretical R-S Latch State Diagram***



### Observed R-S Latch Behavior

 


**Very difficult to observe R-S Latch in the 1-1 state**

**Ambiguously returns to state 0-1 or 1-0**

### A so-called "race condition"

### ***Definition of Terms***

 


**There is a timing "window" around the clocking event during which the input must remain stable and unchanged in order to be recognized**


**Hold Time ( $T_h$ )**  
Minimum time after the clocking event during which the input must remain stable

### **Level-Sensitive Latch** aka Gated R-S Latch

**Schematic:**

 

**Timing Diagram:**

 

## Sequential Switching Networks

Contemporary Logic Design  
Sequential Logic

### Latches vs. Flipflops


#### Input/Output Behavior of Latches and Flipflops

Type	When Inputs are Sampled	When Outputs are Valid
unclocked latch	always	propagation delay from input change
level sensitive latch	clock high ( $T_{su}$ , $T_h$ around falling clock edge)	propagation delay from input change
positive edge flipflop	clock lo-to-hi transition ( $T_{su}$ , $T_h$ around rising clock edge)	propagation delay from rising edge of clock
negative edge flipflop	clock hi-to-lo transition ( $T_{su}$ , $T_h$ around falling clock edge)	propagation delay from falling edge of clock
master/slave flipflop	clock hi-to-lo transition ( $T_{su}$ , $T_h$ around falling clock edge)	propagation delay from falling edge of clock

© R.H. Katz Transparency No. 6-13
 
## Sequential Switching Networks


Contemporary Logic Design  
Sequential Logic



Edge triggered device sample inputs on the event edge

Transparent latches sample inputs as long as the clock is asserted

#### Timing Diagram:

 

Behavior the same unless input changes while the clock is high

© R.H. Katz Transparency No. 6-14


## Sequential Switching Elements

Contemporary Logic Design  
Sequential Logic

### Typical Timing Specifications: Flipflops vs. Latches
 
#### 74LS74 Positive Edge Triggered D Flipflop

- Setup time
- Hold time
- Minimum clock width
- Propagation delays (low to high, high to low, max and typical)



All measurements are made from the clocking event that is, the *rising* edge of the clock

© R.H. Katz Transparency No. 6-15


## Sequential Switching Networks

Contemporary Logic Design  
Sequential Logic

### Typical Timing Specifications: Flipflops vs. Latches
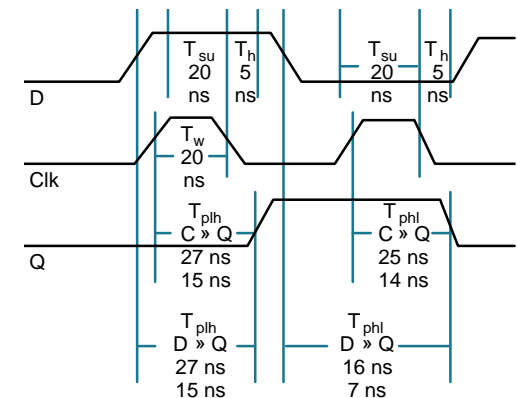
#### 74LS76 Transparent Latch

- Setup time
- Hold time
- Minimum Clock Width
- Propagation Delays: high to low, low to high, maximum, typical data to output clock to output



Measurements from falling clock edge or rising or falling data edge


© R.H. Katz Transparency No. 6-16

## Sequential Switching Elements

### R-S Latch Revisited

Truth Table:  
Next State = F(S, R, Current State)

S(t)	R(t)	Q(t)	Q(t+1)	
0	0	0	0	
0	0	1	1	HOLD
0	1	0	0	
0	1	1	0	RESET
1	0	0	1	
1	0	1	1	SET
1	1	0	X	
1	1	1	X	Not Allowed

 

Derived K-Map:

SR		S			
		00	01	11	10
Q(t)	0	0	0	X	1
	1	1	0	X	1

Characteristic Equation:

$$Q_+ = S + \bar{R} Q_t$$


## Sequential Switching Networks

### J-K Flipflop

How to eliminate the forbidden state?

Idea: use output feedback to guarantee that R and S are never both one

J, K both one yields toggle

 


J(t)	K(t)	Q(t)	Q(t+1)	
0	0	0	0	
0	0	1	1	HOLD
0	1	0	0	
0	1	1	0	RESET
1	0	0	1	
1	0	1	1	SET
1	1	0	1	
1	1	1	0	TOGGLE

Characteristic Equation:

$$Q_+ = Q \bar{K} + \bar{Q} J$$

## Sequential Switching Networks

### J-K Latch: Race Condition

 


Toggle Correctness: Single State change per clocking event

Solution: Master/Slave Flipflop

## Sequential Switching Network


### Master/Slave J-K Flipflop

 

Sample inputs while clock high

Sample inputs while clock low

 Uses time to break feedback path from outputs to inputs!



Correct Toggle Operation


## Sequential Switching Networks

Contemporary Logic Design  
Sequential Logic

### Edge-Triggered Flipflops

**1's Catching:** a 0-1-0 glitch on the J or K inputs leads to a state change! forces designer to use hazard-free logic

**Solution:** edge-triggered logic

 

**Negative edge-triggered FF**  
when clock is high

**Negative Edge-Triggered D flipflop**

4-5 gate delays

setup, hold times  
necessary to successfully  
latch the input

**Characteristic Equation:**  
 $Q^+ = D$


© R.H. Katz Transparency No. 6-21

## Sequential Switching Network


Contemporary Logic Design  
Sequential Logic

### Edge-triggered Flipflops

#### Step-by-step analysis

 

 **Negative edge-triggered FF**  
when clock goes high-to-low  
data is latched




**Negative edge-triggered FF**  
when clock is low  
data is held

© R.H. Katz Transparency No. 6-22

## Sequential Switching Networks

Contemporary Logic Design  
Sequential Logic
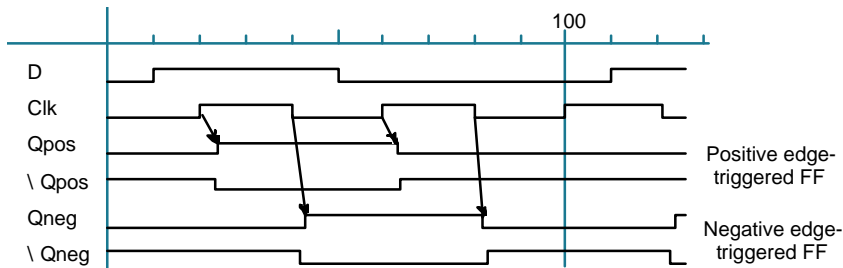
### Positive vs. Negative Edge Triggered Devices



**Positive Edge Triggered**

Inputs sampled on rising edge  
Outputs change after rising edge

**Negative Edge Triggered**

Inputs sampled on falling edge  
Outputs change after falling edge

**Toggle Flipflop**

Formed from J-K with both inputs wired together

© R.H. Katz Transparency No. 6-23

## Timing Methodology

Contemporary Logic Design  
Sequential Logic

### Overview

- Set of rules for interconnecting components and clocks
- When followed, guarantee proper operation of system
- Approach depends on building blocks used for memory elements

**For systems with latches:**

Narrow Width Clocking

Multiphase Clocking (e.g., Two Phase Non-Overlapping)

**For systems with edge-triggered flipflops:**

Single Phase Clocking

- Correct Timing:

- (1) correct inputs, with respect to time, are provided to the FFs
- (2) no FF changes more than once per clocking event

© R.H. Katz Transparency No. 6-24


## Timing Methodologies

Contemporary Logic Design  
Sequential Logic

 
### Cascaded Flipflops and Setup/Hold/Propagation Delays

Shift Register  
S,R are preset, preclear

New value to first stage  
while second stage  
obtains current value  
of first stage



 Correct Operation,  
assuming positive  
edge triggered FF



© R.H. Katz Transparency No. 6-25


## Timing Methodologies

Contemporary Logic Design  
Sequential Logic
 
### Cascaded Flipflops and Setup/Hold/Propagation Delays

Why this works:

- Propagation delays far exceed hold times;  
Clock width constraint exceeds setup time
- This guarantees following stage will latch current value  
before it is replaced by new value
- Assumes infinitely fast distribution of the clock



Timing constraints  
guarantee proper  
operation of  
cascaded components

© R.H. Katz Transparency No. 6-26


## Timing Methodologies

Contemporary Logic Design  
Sequential Logic

### Narrow Width Clocking versus Multiphase Clocking
 
#### Level Sensitive Latches vs. Edge Triggered Flipflops

- Latches use fewer gates to implement a memory function
- Less complex clocking with edge triggered devices



#### CMOS Dynamic Storage Element

Feedback path broken by two  
phases of the clock  
(just like master/slave idea!)

8 transistors to implement memory function

but requires two clock signals constrained  
to be non-overlapping

Edge-triggered D-FF: 6 gates (5 x 2-input, 1 x 3-input) = 26 transistors!

© R.H. Katz Transparency No. 6-27


## Timing Methodologies

Contemporary Logic Design  
Sequential Logic
 
### Narrow Width Clocking for Systems with Latches for State

Generic Block Diagram  
for Clocked Sequential  
System

state implemented by  
latches or edge-triggered FFs



Two-sided Constraints:  
must be careful of very fast signals as well as very slow signals!



Clock Width < fastest propagation through comb. logic  
plus latch prop delay

Clock Period > slowest propagation through comb. logic  
(rising edge to rising edge)

© R.H. Katz Transparency No. 6-28



## Timing Methodologies

Contemporary Logic Design  
Sequential Logic

### Two Phase Non-Overlapped Clocking

Clock Waveforms:  
must never overlap!

only worry about slow signals

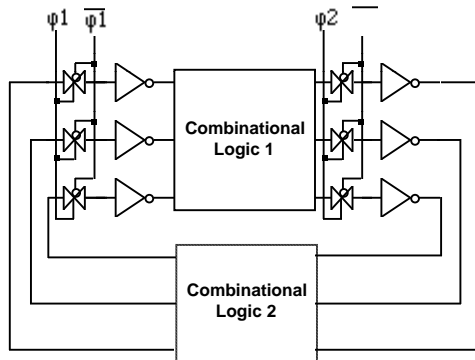 

**Embedding CMOS storage element into Clocked Sequential Logic**

Note that Combinational Logic can be partitioned into two pieces

C/L1: inputs latched and stable by end of phase 1; compute between phases, latch outputs by end of phase 2


C/L2: just the reverse

© R.H. Katz Transparency No. 6-29

## Timing Methodologies

Contemporary Logic Design  
Sequential Logic
 
### Generating Two-Phase Non-Overlapping Clocks




**Single reference clock (or crystal)**

Phase 1 high while clock is low

Phase 2 high while clock is high

 Phase X cannot go high until phase Y goes low!



Non-overlap time can be increased by increasing the delay on the feedback path

© R.H. Katz Transparency No. 6-30

## Timing Methodologies

Contemporary Logic Design  
Sequential Logic


### The Problem of Clock Skew

Correct behavior assumes next state of all storage elements determined by all storage elements *at the same time*

Not possible in real systems!

- logical clock driven from more than one physical circuit with timing behavior
- different wire delay to different points in the circuit

Effect of Skew on Cascaded Flipflops:

 

Original State: Q0 = 1, Q1 = 1, In = 0  
Because of skew, next state becomes: Q0 = 0, Q1 = 0,  
not Q0 = 0, Q1 = 1

© R.H. Katz Transparency No. 6-31

## Timing Methodologies

Contemporary Logic Design  
Sequential Logic

### Design Strategies for Minimizing Clock Skew

Typical propagation delays for LS FFs: 13 ns

Need substantial clock delay (on the order of 13 ns) for skew to be a problem in this relatively slow technology

Nevertheless, the following are good design practices:

- distribute clock signals in general direction of data flows
- wire carrying the clock between two communicating components should be as short as possible
- for multiphase clocked systems, distribute all clocks in similar wire paths; this minimizes the possibility of overlap
- for the non-overlap clock generate, use the phase feedback signals from the furthest point in the circuit to which the clock is distributed; this guarantees that the phase is seen as low everywhere before it allows the next phase to go high

© R.H. Katz Transparency No. 6-32



## Realizing Circuits with Different Kinds of FFs

Contemporary Logic Design  
Sequential Logic

### Choosing a Flipflop

**R-S Clocked Latch:**  
used as storage element in narrow width clocked systems  
its use is not recommended!  
however, fundamental building block of other flipflop types

**J-K Flipflop:**  
versatile building block  
can be used to implement D and T FFs  
usually requires least amount of logic to implement  $f(\text{In}, Q, Q+)$   
but has two inputs with increased wiring complexity

because of 1's catching, never use master/slave J-K FFs  
edge-triggered varieties exist

**D Flipflop:**  
minimizes wires, much preferred in VLSI technologies  
simplest design technique  
best choice for storage registers

**T Flipflops:**  
don't really exist, constructed from J-K FFs  
usually best choice for implementing counters

Preset and Clear inputs highly desirable!!

© R.H. Katz Transparency No. 6-33

## Realizing Circuits with Different Kinds of Flipflops

Contemporary Logic Design  
Sequential Logic

### Characteristic Equations

R-S:  $Q+ = S + \bar{R}Q$

D:  $Q+ = D$


J-K:  $Q+ = J\bar{Q} + \bar{K}Q$

T:  $Q+ = T\bar{Q} + \bar{T}Q$

Derived from the K-maps  
for  $Q+ = f(\text{Inputs}, Q)$

E.g., J=K=0, then  $Q+ = Q$   
J=1, K=0, then  $Q+ = 1$   
J=0, K=1, then  $Q+ = 0$   
J=1, K=1, then  $Q+ = \bar{Q}$
 
### Implementing One FF in Terms of Another



© R.H. Katz Transparency No. 6-34

## Realizing Circuits with Different Kinds of Flipflops

Contemporary Logic Design  
Sequential Logic

### Design Procedure


**Excitation Tables:** What are the necessary inputs to cause a particular kind of change in state?

Q	Q+	R	S	J	K	T	D
0	0	X	0	0	X	0	0
0	1	0	1	1	X	1	1
1	0	1	0	X	1	1	0
1	1	0	X	X	0	0	1

Implementing D FF with a J-K FF:

 - 1) Start with K-map of  $Q+ = f(D, Q)$
- 2) Create K-maps for J and K with same inputs (D, Q)
- 3) Fill in K-maps with appropriate values for J and K to cause the same state changes as in the original K-map

E.g., D = Q = 0,  $Q+ = 0$   
then J = 0, K = X



© R.H. Katz Transparency No. 6-35

## Realizing Circuits with Different Kinds of Flipflops


Contemporary Logic Design  
Sequential Logic

### Design Procedure (Continued)

Implementing J-K FF with a D FF:

 1) K-Map of  $Q+ = F(J, K, Q)$

2,3) Revised K-map using D's excitation table  
its the same! that is why design procedure with D FF is simple!



$$Q+ = D = J\bar{Q} + \bar{K}Q$$

Resulting equation is the combinational logic input to D to cause same behavior as J-K FF. Of course it is identical to the characteristic equation for a J-K FF.

© R.H. Katz Transparency No. 6-36

## Metastability and Asynchronous Inputs

Contemporary Logic Design  
Sequential Logic

### Terms and Definitions

#### Clocked synchronous circuits

- common reference signal called the clock
- state of the circuit changes in relation to this clock signal

#### Asynchronous circuits

- inputs, state, and outputs sampled or changed independent of a common reference signal

R-S latch is asynchronous, J-K master/slave FF is synchronous

#### Synchronous inputs

- active only when the clock edge or level is active

#### Asynchronous inputs

- take effect immediately, without consideration of the clock

Compare R, S inputs of clocked transparent latch vs. plain latch

© R.H. Katz Transparency No. 6-37

## Metastability and Asynchronous Inputs

Contemporary Logic Design  
Sequential Logic

### Asynchronous Inputs Are Dangerous!

Since they take effect immediately, glitches can be disastrous

Synchronous inputs are greatly preferred!


But sometimes, asynchronous inputs cannot be avoided  
e.g., reset signal, memory wait signal

© R.H. Katz Transparency No. 6-38

## Metastability and Asynchronous Outputs

Contemporary Logic Design  
Sequential Logic

### Handling Asynchronous Inputs

 


Never allow asynchronous inputs to be fanned out to more than one FF within the synchronous system

© R.H. Katz Transparency No. 6-39

## Metastability and Asynchronous Inputs

Contemporary Logic Design  
Sequential Logic

### What Can Go Wrong

 


Single FF that receives the asynchronous signal is a synchronizer

© R.H. Katz Transparency No. 6-40

## Metastability and Asynchronous Inputs


Contemporary Logic Design  
Sequential Logic

### Synchronizer Failure

 


When FF input changes close to clock edge, the FF may enter the *metastable* state: neither a logic 0 nor a logic 1

 It may stay in this state an indefinite amount of time, although this is not likely in real circuits



 Small, but non-zero probability that the FF output will get stuck in an in-between state



Oscilloscope Traces Demonstrating Synchronizer Failure and Eventual Decay to Steady State


© R.H. Katz Transparency No. 6-41

## Metastability and Asynchronous Inputs

Contemporary Logic Design  
Sequential Logic
 
### Solutions to Synchronizer Failure

- the probability of failure can never be reduced to 0, but it can be reduced
- slow down the system clock  
this gives the synchronizer more time to decay into a steady state  
synchronizer failure becomes a big problem for very high speed systems
- use fastest possible logic in the synchronizer  
this makes for a very sharp "peak" upon which to balance  
S or AS TTL D-FFs are recommended
- cascade two synchronizers



© R.H. Katz Transparency No. 6-42

## Self-Timed and Speed Independent Circuits


Contemporary Logic Design  
Sequential Logic

### Limits of Synchronous Systems


Fully synchronous not possible for very large systems because of problems of clock skew

Partition system into components that are locally clocked

 These communicate using "speed independent" protocols



### Request/Acknowledgement Signaling

 


© R.H. Katz Transparency No. 6-43


## Self-Timed and Speed Independent Circuits

Contemporary Logic Design  
Sequential Logic

### Synchronous Signaling

 

 Master issues read request; Slave produces data and acks back



### Alternative Synchronous Scheme:

Slave issues WAIT signal if it cannot satisfy request in one clock cycle

© R.H. Katz Transparency No. 6-44

### Self-Timed and Speed Independent Circuits


Contemporary Logic Design  
Sequential Logic

#### *Asynchronous/Speed Independent Signaling*

Communicate information by signal levels rather than edges!

No clock signal
 
#### *4 Cycle Signaling/Return to Zero Signaling*



- (1) master raises request  
slave performs request
- (2) slave "done" by raising  
acknowledge
- (3) master latches data  
acks by lowering request
- (4) slave resets self by lowing  
acknowledge signal


© R.H. Katz Transparency No. 6-45

### Self-Timed and Speed Independent Circuits

Contemporary Logic Design  
Sequential Logic

#### *Alternative: 2 cycle signaling*

Non-Return-to-Zero

 

- (1) master raises request  
slave services request
- (2) slave indicates that it is  
done by raising acknowledge

Next request indicated by low level of request

Requires additional state in master and slave  
to remember previous setting or request/acknowledge

4 Cycle Signaling is more foolproof

© R.H. Katz Transparency No. 6-46

### Self-Timed and Speed Independent Circuits


Contemporary Logic Design  
Sequential Logic

#### *Self-Timed Circuits*

Determine on their own when a given request has been serviced

No internal clocks

 Usually accomplished by modeling worst case delay within  
self-timed component



Models worst case delay  
e.g., if combinational logic is 5 gate levels deep,  
delay line between request in and ack out is  
also 5 levels deep

© R.H. Katz Transparency No. 6-47

### Chapter Summary

Contemporary Logic Design  
Sequential Logic

- Fundamental Building Block of Circuits with State: latch and flipflop
- R-S Latch, J-K master/slave Flipflop, Edge-triggered D Flipflop
- Clocking Methodologies:
  - For latches: Narrow width clocking vs. Multiphase Non-overlapped
  - Narrow width clocking and two sided timing constraints
  - Two phase clocking and single sided timing constraints
  - For FFs: Single phase clocking with edge triggered flipflops
  - Cascaded FFs work because propagation delays exceed hold times
  - Beware of Clock Skew
- Asynchronous Inputs and Their Dangers
  - Synchronizer Failure: What it is and how to minimize its impact
- Speed Independent Circuits
  - Asynchronous Signaling Conventions: 4 and 2 Cycle Handshakes
  - Self-Timed Circuits

© R.H. Katz Transparency No. 6-48