

Chapter #7: Sequential Logic Case Studies

Contemporary Logic Design

Randy H. Katz
University of California, Berkeley

June 1993

Motivation

- **Flipflops:** most primitive "packaged" sequential circuits
- **More complex sequential building blocks:**
Storage registers, Shift registers, Counters
Available as components in the TTL Catalog
- **How to represent and design simple sequential circuits:** counters
- **Problems and pitfalls when working with counters:**
Start-up States
Asynchronous vs. Synchronous logic

Chapter Overview

Examine Real Sequential Logic Circuits Available as Components

- Registers for storage and shifting
- Random Access Memories
- Counters

Counter Design Procedure

- Simple but useful finite state machine
- State Diagram, State Transition Table, Next State Functions
- Excitation Tables for implementation with alternative flipflop types


Synchronous vs. Asynchronous Counters

- Ripple vs. Synchronous Counters
- Asynchronous vs. Synchronous Clears and Loads

Kinds of Registers and Counters


Storage Register

 Group of storage elements read/written as a unit



4-bit register constructed from 4 D FFs
Shared clock and clear lines

Schematic Shape

 


TTL 74171 Quad D-type FF with Clear
(Small numbers represent pin #s on package)

Kinds of Registers and Counters

Contemporary Logic Design
Sequential Case Studies


Input/Output Variations

 Selective Load Capability
Tri-state or Open Collector Outputs
True and Complementary Outputs



74377 Octal D-type FFs
with input enable

 *EN enabled low and
lo-to-hi clock transition
to load new data into
register*



74374 Octal D-type FFs
with output enable

*OE asserted low
presents FF state to
output pins; otherwise
high impedance*


© R.H. Katz Transparency No. 7-5

Kinds of Registers and Counters

Contemporary Logic Design
Sequential Case Studies

Register Files

 Two dimensional array of flipflops
Address used as index to a particular word
Word contents read or written



74670 4x4 Register File with
Tri-state Outputs

Separate Read and Write Enables
Separate Read and Write Address
Data Input, Q Outputs

Contains 16 D-ffs, organized as
four rows (words) of four elements (bits)



© R.H. Katz Transparency No. 7-6

Kinds of Registers and Counters

Contemporary Logic Design
Sequential Case Studies


Shift Registers

  Storage + ability to circulate data among storage elements



Shift from left storage
element to right neighbor
on every lo-to-hi transition
on shift signal

 Wrap around from rightmost
element to leftmost element



*Master Slave FFs: sample inputs while
clock is high; change outputs on
falling edge*


© R.H. Katz Transparency No. 7-7

Kinds of Registers and Counters

Contemporary Logic Design
Sequential Case Studies

Shift Register I/O

 Serial vs. Parallel Inputs
Serial vs. Parallel Outputs
Shift Direction: Left vs. Right



74194 4-bit Universal
Shift Register

Serial Inputs: LSI, RSI
Parallel Inputs: D, C, B, A
Parallel Outputs: QD, QC, QB, QA
Clear Signal
Positive Edge Triggered Devices

S1, S0 determine the shift function

*S1 = 1, S0 = 1: Load on rising clk edge
synchronous load*

*S1 = 1, S0 = 0: shift left on rising clk edge
LSI replaces element D*

*S1 = 0, S0 = 1: shift right on rising clk edge
RSI replaces element A*

S1 = 0, S0 = 0: hold state

Multiplexing logic on input to each FF!


Shifters well suited for serial-to-parallel conversions,
such as terminal to computer communications

© R.H. Katz Transparency No. 7-8

Kinds of Registers and Counters

Contemporary Logic Design
Sequential Case Studies

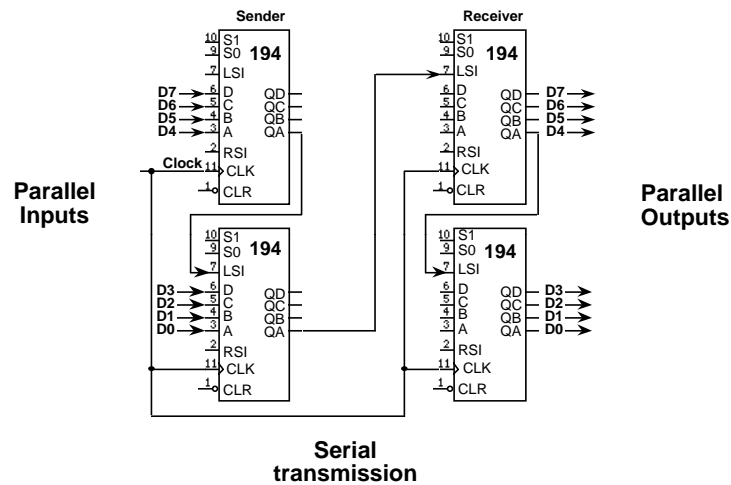Shift Register Application: Parallel to Serial Conversion



© R.H. Katz Transparency No. 7-9

Kinds of Registers and Counters

Contemporary Logic Design
Sequential Case Studies

Counters

Proceed through a well-defined sequence of states in response to count signal

3 Bit Up-counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, ...

3 Bit Down-counter: 111, 110, 101, 100, 011, 010, 001, 000, 111, ...

Binary vs. BCD vs. Gray Code Counters


A counter is a "degenerate" finite state machine/sequential circuit where the state *is* the only output

© R.H. Katz Transparency No. 7-10

Kinds of Registers and Counters

Contemporary Logic Design
Sequential Case Studies

Johnson (Mobius) Counter

 


8 possible states, single bit change per state, useful for avoiding glitches

© R.H. Katz Transparency No. 7-11

Kinds of Registers and Counters

Contemporary Logic Design
Sequential Case Studies

Catalog Counter

 

74163 Synchronous
4-Bit Upcounter

Synchronous Load and Clear Inputs

Positive Edge Triggered FFs

Parallel Load Data from D, C, B, A

P, T Enable Inputs: both must be asserted to enable counting

RCO: asserted when counter enters its highest state 1111, used for cascading counters
"Ripple Carry Output"


74161: similar in function, asynchronous load and reset

© R.H. Katz Transparency No. 7-12

Kinds of Registers and Counters

74163 Detailed Timing Diagram

 Contemporary Logic Design
Sequential Case Studies



© R.H. Katz Transparency No. 7-13

Counter Design Procedure


Contemporary Logic Design
Sequential Case Studies

Introduction

This procedure can be generalized to implement ANY finite state machine

Counters are a very simple way to start:
no decisions on what state to advance to next
current state is the output

Example: 3-bit Binary Upcounter

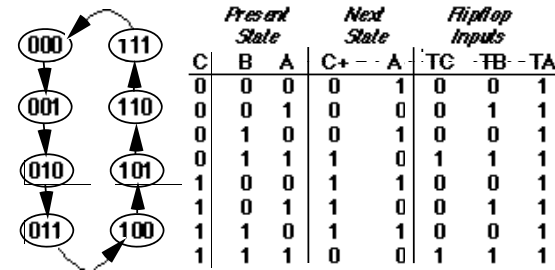

State Transition Table

Flipflop Input Table

Decide to implement with Toggle Flipflops

What inputs must be presented to the T FFs to get them to change to the desired state bit?

This is called "Remapping the Next State Function"

© R.H. Katz Transparency No. 7-14


Counter Design Procedure

Introduction

This procedure can be generalized to implement ANY finite state machine

Counters are a very simple way to start:
no decisions on what state to advance to next
current state is the output

Example: 3-bit Binary Upcounter

 

State Transition Table

Flipflop Input Table

Decide to implement with Toggle Flipflops

What inputs must be presented to the T FFs to get them to change to the desired state bit?

This is called "Remapping the Next State Function"

© R.H. Katz Transparency No. 7-15

Counter Design Procedure

Contemporary Logic Design
Sequential Case Studies

Example Continued

K-maps for Toggle Inputs:

CB	A			
	00	01	11	10
0				
1				

TA =

CB	A			
	00	01	11	10
0				
1				

TB =

CB	A			
	00	01	11	10
0				
1				

TC =




Resulting Logic Circuit:

© R.H. Katz Transparency No. 7-16


Counter Design Procedure

Example Continued


K-maps for Toggle Inputs:

   

Resulting Logic Circuit:

 

Timing Diagram:

 


Counter Design Procedure

More Complex Count Sequence

Step 1: Derive the State Transition Diagram

Count sequence: 000, 010, 011, 101, 110

 

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			


Step 2: State Transition Table

Counter Design Procedure

More Complex Count Sequence

Step 1: Derive the State Transition Diagram

Count sequence: 000, 010, 011, 101, 110

 

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	
0	0	1	X	X	
0	1	0	0	1	
0	1	1	1	0	
1	0	0	X	X	
1	0	1	1	1	
1	1	0	0	0	
1	1	1	X	X	


Step 2: State Transition Table

Note the Don't Care conditions

Counter Design Procedure

More Complex Count Sequence


Step 3: K-Maps for Next State Functions

 

Counter Design Procedure

More Complex Count Sequence

Step 3: K-Maps for Next State Functions

 

Counter Design Procedure

More Complex Counter Sequencing

Step 4: Choose Flipflop Type for Implementation Use Excitation Table to Remap Next State Functions

			Present State			Toggle Inputs		
			C	B	A	TC	B	A
Q	Q+	T	0	0	0			
0	0	0	0	0	1			
0	1	1	0	1	0			
1	0	1	0	1	1			
1	1	0	1	0	0			
Toggle Excitation Table			1	0	1			
			1	0	1			
			1	1	0			
			1	1	1			
			Remapped Next State Functions					

Counter Design Procedure

More Complex Counter Sequencing

Step 4: Choose Flipflop Type for Implementation Use Excitation Table to Remap Next State Functions


			Present State			Toggle Inputs		
			C	B	A	TC	TB	TA
Q	Q+	T	0	0	0	0	1	0
0	0	0	0	0	1	X	X	X
0	1	1	0	1	0	0	0	1
1	0	1	0	1	1	1	1	0
1	1	0	1	0	0	X	X	X
Toggle Excitation Table			1	0	1	0	1	1
			1	1	0	1	1	0
			1	1	1	X	X	X
			1	1	1	X	X	X

Remapped Next State Functions

Counter Design Procedure

More Complex Counter Sequencing

Remapped K-Maps

 

$$TC = \bar{A}C + A\bar{C} = A \text{ xor } C$$

$$TB = A + \bar{B} + C$$

$$TA = \bar{A}B\bar{C} + \bar{B}C$$


Counter Design Procedure

More Complex Counter Sequencing


Resulting Logic:

5 Gates

13 Input Literals +
Flipflop connections

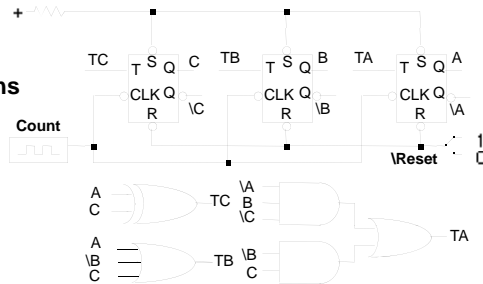

Timing Waveform:

 

© R.H. Katz Transparency No. 7-27

Self-Starting Counters

Start-Up States


At power-up, counter may be in possible state

Designer must guarantee that it (eventually) enters a valid state

Especially a problem for counters that validly use a subset of states

Self-Starting Solution:

 Design counter so that even the invalid states
eventually transition to valid state




Implementation
in Previous
Slide!

Two Self-Starting State Transition Diagrams
for the Example Counter

© R.H. Katz Transparency No. 7-28

Self-Starting Counters

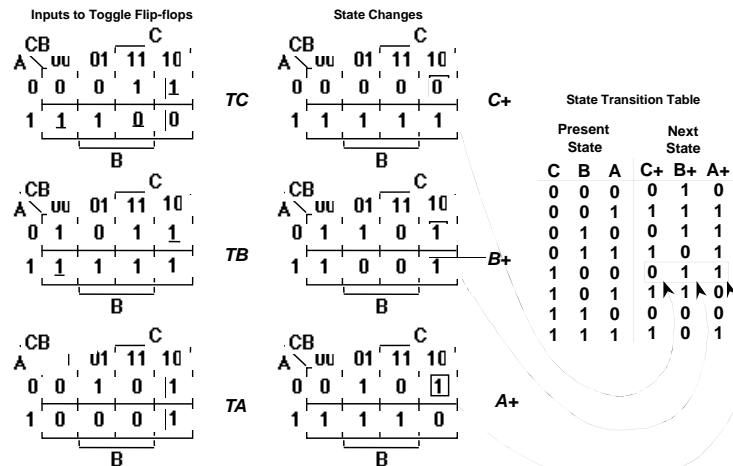Deriving State Transition Table from Don't Care Assignment



© R.H. Katz Transparency No. 7-29

Implementation with Different Kinds of FFs

R-S Flipflops

Continuing with the 000, 010, 011, 101, 110, 000, ... counter example

Present State				Next State			Remapped Next State					
Q	Q+	R	S	C+	B+	A+	RC	SC	RB	SB	R/	SA
0	0	X	0	0	1	0	X	0	0	1	X	0
0	1	0	1	X	X	X	X	X	X	X	X	X
1	0	1	0	0	1	1	X	0	0	X	0	1
1	1	0	X	1	0	1	0	1	1	0	0	X
1	0	1	1	X	X	X	X	X	X	X	X	X
1	0	1	1	1	1	0	0	X	0	1	1	0
1	1	0	0	0	0	0	1	0	1	0	X	0
1	1	1	1	X	X	X	X	X	X	X	X	X

Remapped Next State Functions

© R.H. Katz Transparency No. 7-30

Implementation with Different Kinds of FFs

RS FFs Continued

CB	00	01	11	10
A				
0				
1				

RC

CB	00	01	11	10
A				
0				
1				

SC

CB	00	01	11	10
A				
0				
1				

RB

CB	00	01	11	10
A				
0				
1				

SB

CB	00	01	11	10
A				
0				
1				

RA

CB	00	01	11	10
A				
0				
1				

SA

Contemporary Logic Design
Sequential Case Studies

RC =

SC =

RB =

SB =

RA =

SA =

© R.H. Katz Transparency No. 7-32

Implementation with Different Kinds of FFs

RS FFs Continued

CB	00	01	11	10
A				
0	X	X	1	X
1	X	0	X	0

B

CB	00	01	11	10
A				
0	0	0	0	X
1	X	1	X	X

B

CB	00	01	11	10
A				
0	0	0	1	X
1	X	1	X	0

B

CB	00	01	11	10
A				
0	1	X	0	X
1	X	0	X	1

B

CB	00	01	11	10
A				
0	X	0	X	X
1	X	0	X	1

B

CB	00	01	11	10
A				
0	0	1	0	X
1	X	X	X	0

B

RC = \bar{A}

SC = A

RB = $A B + B C$

SB = \bar{B}


RA = C

SA = $\bar{B} C$

© R.H. Katz Transparency No. 7-33

Implementation With Different Kinds of FFs

RS FFs Continued

 

Resulting Logic Level Implementation:
3 Gates, 11 Input Literals + Flipflop connections

Contemporary Logic Design
Sequential Case Studies

© R.H. Katz Transparency No. 7-34

Implementation with Different FF Types

J-K FFs

				Present State			Next State			Remapped Next State							
Q	Q+	J	K	C	B	A	C+	B+	A+	J	K	JB	KB	JA	KA		
0	0	0	X	0	0	0	0	1	0	0	X	1	X	0	X		
0	1	1	X	0	0	1	X	X	X	X	X	X	X	X	X		
1	0	X	1	0	1	0	0	1	1	0	X	X	0	1	X		
1	1	X	0	0	1	1	1	0	1	1	X	X	1	X	0		
$Q+ = J\overline{Q} + \overline{K}Q$ J-K Excitation Table				1	0	0	X	X	X	X	X	X	X	X	X	X	
				1	0	1	1	1	0	X	0	1	X	X	0	X	1
				1	1	0	0	0	0	X	1	X	1	0	X	0	X
				1	1	1	X	X	X	X	X	X	X	X	X	X	X

$Q+ = JQ + \bar{K}Q$
J-K Excitation Table

Remapped Next State Functions

Contemporary Logic Design
Sequential Case Studies

© R.H. Katz Transparency No. 7-35

Implementation with Different FF Types

J-K FFs Continued

A \ CB	00	01	11	10
0				
1				

JC

A \ CB	00	01	11	10
0				
1				

KC

A \ CB	00	01	11	10
0				
1				

JB

A \ CB	00	01	11	10
0				
1				

KB

A \ CB	00	01	11	10
0				
1				

JA

A \ CB	00	01	11	10
0				
1				

KA

JC =

KC =

JB =

KB =

JA =

KA =

Implementation with Different FF Types

J-K FFs Continued

A \ CB	00	01	11	10
0	0	0	X	X
1	X	1	X	X

JC

B

A \ CB	00	01	11	10
0	X	X	1	X
1	X	X	X	0

KC

B

A \ CB	00	01	11	10
0	1	X	X	X
1	X	X	X	1

JB

B

A \ CB	00	01	11	10
0	X	0	1	X
1	X	1	X	X

KB

B

A \ CB	00	01	11	10
0	0	1	0	X
1	X	X	X	X

JA

B

A \ CB	00	01	11	10
0	X	X	X	X
1	X	0	X	1

KA

B

JC = A

KC = \bar{A}

JB = 1


KB = A + C

JA = B \bar{C}

KA = C

Implementation with Different FF Types

J-K FFs Continued

 

Resulting Logic Level Implementation:
2 Gates, 10 Input Literals + Flipflop Connections

Implementation with Different FF Types


D FFs

Simplest Design Procedure: No remapping needed!

DC = A

DB = $\bar{A} \bar{C} + \bar{B}$

DA = B \bar{C}

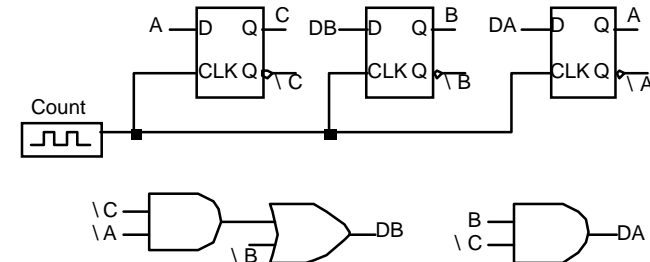

Resulting Logic Level Implementation:
3 Gates, 8 Input Literals + Flipflop connections

Implementation with Different FF Types

Contemporary Logic Design
Sequential Case Studies

Comparison

- T FFs well suited for straightforward binary counters
But yielded worst gate and literal count for this example!
- No reason to choose R-S over J-K FFs: it is a proper subset of J-K
R-S FFs don't really exist anyway
J-K FFs yielded lowest gate count
Tend to yield best choice for packaged logic where gate count is key
- D FFs yield simplest design procedure
Best literal count
D storage devices very transistor efficient in VLSI
Best choice where area/literal count is the key


© R.H. Katz Transparency No. 7-41

Asynchronous vs. Synchronous Counters


Contemporary Logic Design
Sequential Case Studies

Ripple Counters

 Deceptively attractive alternative to synchronous design style



Count signal ripples from left to right

 

State transitions are not sharp!



Can lead to "spiked outputs" from combinational logic decoding the counter's state

© R.H. Katz Transparency No. 7-42

Asynchronous vs. Synchronous Counters

Contemporary Logic Design
Sequential Case Studies

 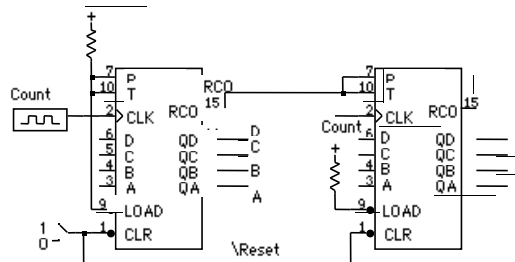Cascaded Synchronous Counters with Ripple Carry Outputs



First stage RCO enables second stage for counting

RCO asserted soon after stage enters state 1111

also a function of the T Enable

Downstream stages lag in their 1111 to 0000 transitions

Affects Count period and decoding logic

© R.H. Katz Transparency No. 7-43


Asynchronous vs. Synchronous Counters

Contemporary Logic Design
Sequential Case Studies


The Power of Synchronous Clear and Load

Starting Offset Counters:

 e.g., 0110, 0111, 1000, 1001, 1010, 1011, 1100, 1101, 1111, 0110, ...



0110 is the state to be loaded

 

Use RCO signal to trigger Load of a new state

Since 74163 Load is synchronous, state changes only on the next rising clock edge

© R.H. Katz Transparency No. 7-44


Asynchronous vs. Synchronous Counters

Contemporary Logic Design
Sequential Case Studies


Offset Counters Continued

Ending Offset Counter:

 
e.g., 0000, 0001, 0010, ..., 1100, 1101, 0000



 Decode state to determine when to reset to 0000



 Clear signal takes effect on the rising count edge



Replace '163 with '161, Counter with Async Clear
Clear takes effect immediately!

© R.H. Katz Transparency No. 7-45

Random Access Memories

Contemporary Logic Design
Sequential Case Studies


Static RAM

Transistor efficient methods for implementing storage elements

Small RAM: 256 words by 4-bit

Large RAM: 4 million words by 1-bit

We will discuss a 1024 x 4 organization

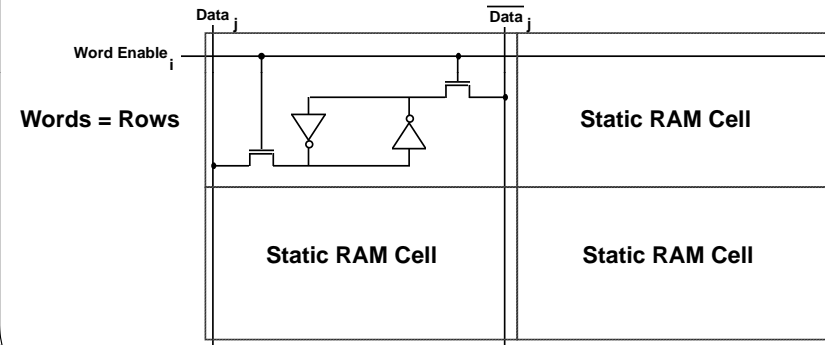

Columns = Bits (Double Rail Encoded)

© R.H. Katz Transparency No. 7-46

Random Access Memories

Contemporary Logic Design
Sequential Case Studies


Static RAM Organization

Chip Select Line (active lo)

Write Enable Line (active lo)

10 Address Lines

4 Bidirectional Data Lines

 


© R.H. Katz Transparency No. 7-47

Random Access Memories

Contemporary Logic Design
Sequential Case Studies

RAM Organization

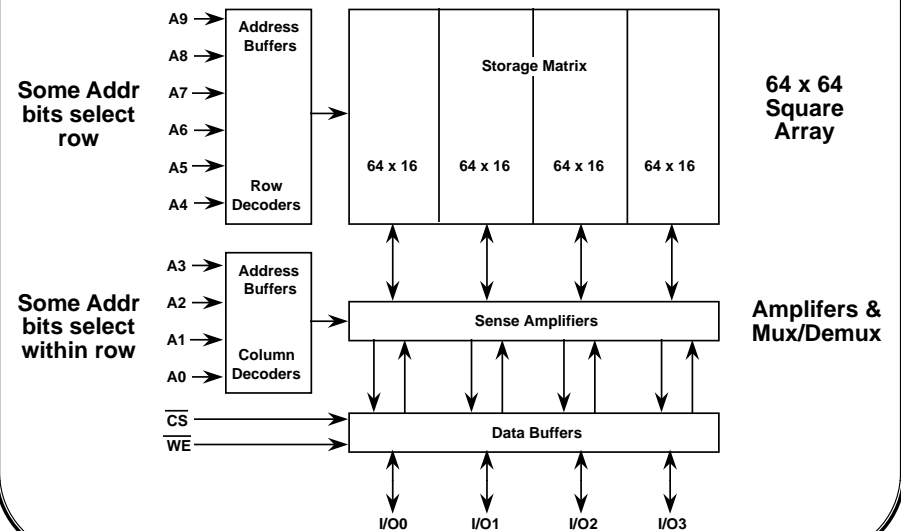Long thin layouts are not the best organization for a RAM




© R.H. Katz Transparency No. 7-48


Random Access Memories

RAM Timing

Simplified Read Timing

 


Simplified Write Timing

 

© R.H. Katz Transparency No. 7-49

Random Access Memories

Dynamic RAMs

 

1 Transistor (+ capacitor) memory element

Read: Assert Word Line, Sense Bit Line

Write: Drive Bit Line, Assert Word Line

Destructive Read-Out

Need for Refresh Cycles: storage decay in ms

Internal circuits read word and write back

© R.H. Katz Transparency No. 7-50

Random Access Memories

DRAM Organization


Long rows to simplify refresh

Two new signals: RAS, CAS

Row Address Strobe

Column Address Strobe

replace Chip Select

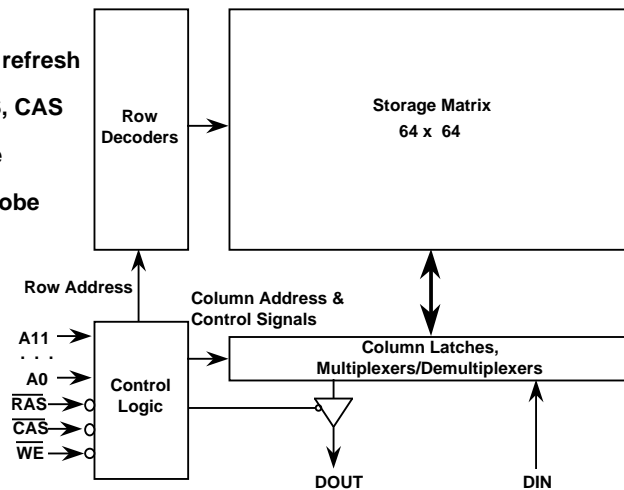


© R.H. Katz Transparency No. 7-51

Random Access Memory

RAS, CAS Addressing

Even to read 1 bit, an entire 64-bit row is read!

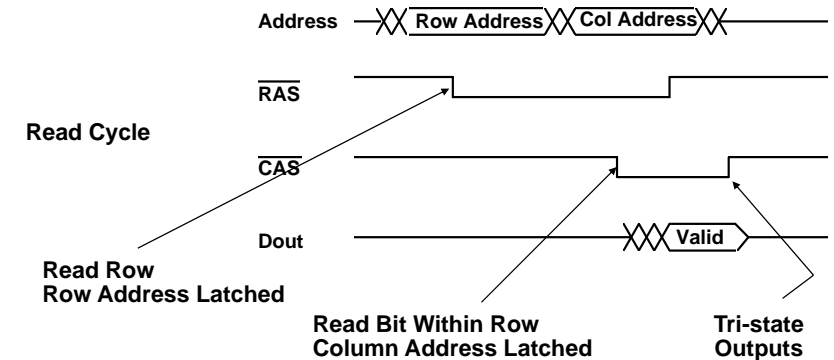Separate addressing into two cycles: Row Address, Column Address
Saves on package pins, speeds RAM access for sequential bits!




© R.H. Katz Transparency No. 7-52

Random Access Memory

Write Cycle Timing

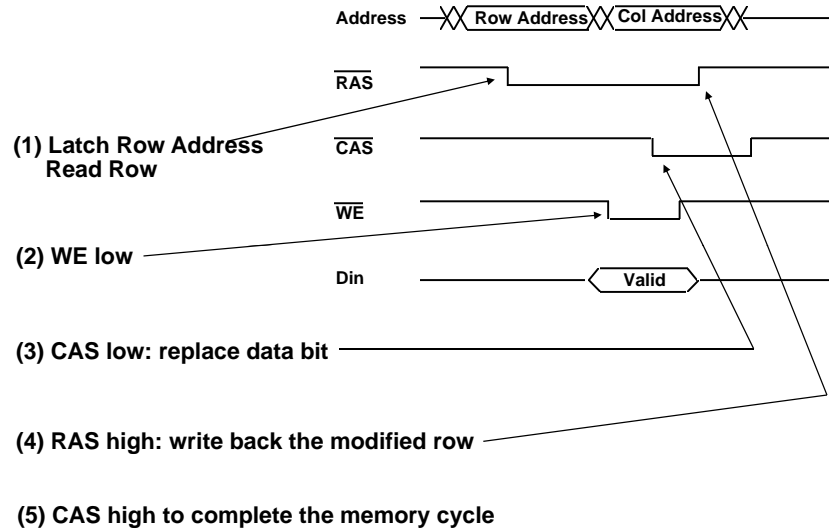Contemporary Logic Design
Sequential Case Studies



© R.H. Katz Transparency No. 7-53

Random Access Memory

RAM Refresh

Contemporary Logic Design
Sequential Case Studies

Refresh Frequency:

4096 word RAM -- refresh each word once every 4 ms

Assume 120ns memory access cycle

This is one refresh cycle every 976 ns (1 in 8 DRAM accesses)!

But RAM is really organized into 64 rows

This is one refresh cycle every 62.5 μ s (1 in 500 DRAM accesses)

Large capacity DRAMs have 256 rows, refresh once every 16 μ s

RAS-only Refresh (RAS cycling, no CAS cycling)

External controller remembers last refreshed row

Some memory chips maintain refresh row pointer

CAS before RAS refresh: if CAS goes low before RAS, then refresh

© R.H. Katz Transparency No. 7-54

Random Access Memory

DRAM Variations

Contemporary Logic Design
Sequential Case Studies

Page Mode DRAM:

read/write bit within last accessed row without RAS cycle

RAS, CAS, CAS, . . ., CAS, RAS, CAS, ...

New column address for each CAS cycle

Static Column DRAM:

like page mode, except address bit changes signal new cycles rather than CAS cycling

on writes, deselect chip or CAS while address lines are changing

Nibble Mode DRAM:

like page mode, except that CAS cycling implies next column address in sequence -- no need to specify column address after first CAS

Works for 4 bits at a time (hence "nibble")

RAS, CAS, CAS, CAS, CAS, RAS, CAS, CAS, CAS, CAS, . . .

© R.H. Katz Transparency No. 7-55

Chapter Summary

Contemporary Logic Design
Sequential Case Studies

- The Variety of Sequential Circuit Packages
Registers, Shifters, Counters, RAMs
 - Counters as Simple Finite State Machines
 - Counter Design Procedure
 1. Derive State Diagram
 2. Derive State Transition Table
 3. Determine Next State Functions
 4. Remap Next State Functions for Target FF Types
Using Excitation Tables; Implement Logic
 - Different FF Types in Counters
J-K best for reducing gate count in packaged logic
D is easiest design plus best for reducing wiring and area in VLSI
 - Asynchronous vs. Synchronous Counters
Avoid Ripple Counters! State transitions are not sharp
Beware of potential problems when cascading synchronous counters
- Offset counters: easy to design with synchronous load and clear
Never use counters with asynchronous clear for this kind of application

© R.H. Katz Transparency No. 7-56